

Department of  
**Electronic & Telecommunication Engineering**

**LAB MANUAL**

**VLSI LAB**

**B.Tech– VI Semester**



**KCT College OF ENGG AND TECH.**

**VILLAGE FATEHGARH**

**DISTT.SANGRUR**


**List of Experiments:**

1. Design of basic Gates: AND, OR, NOT.
2. Design of universal gates.
3. Design of 8:1 Mux using other basic gates.
4. Design of 2 to 4 Decoder.
5. Design of Half-Adder, Full Adder, Half Subtractor, Full Subtractor.
6. Design of 3:8 Decoder.
7. Design of 8:3 Priority Encoder.
8. Design of 4 Bit Binary to Grey code Converter.
9. Design of 4 Bit Binary to BCD Converter using sequential statement.
10. Design an 8 Bit parity generator ( with for loop and Generic statements).
11. Design of 2,s Complementary for 8-bit Binary number using Generate statements.

**Sequential Design Exercises**

12. Design of all type of Flip-Flops using ( if-then-else) Sequential Constructs.
13. Design of 8-Bit Shift Register with shift Right, Rhisft Left, Load and Synchronous reset.
14. Design of Synchronous 8-bit Johnson Counter.
15. Design of Synchronous 8-Bit universal shift register ( parallel-in, parallel-out) with 3-state output ( IC 74299)
16. Design of 4 Bit Binary to BCD Converter using sequential statement.
17. Design counters (MOD 3, MOD 5, MOD 8, MOD 16)
18. Design a decimal up/down counter that counts up from 00 to 99 or down from 99 to 00.
19. Design 3-line to 8-line decoder with address latch.

**Schematic Diagram:**

 

**Experiment No:1&2****Logic Gates**

---

**Aim:** To Design Logic Gates using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

**VHDL Code:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity logic_gates is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          AND1 : out STD_LOGIC;
          OR1 : out STD_LOGIC;
          NOT1 : out STD_LOGIC;
          XOR1 : out STD_LOGIC;
          NAND1 : out STD_LOGIC;
          NOR1 : out STD_LOGIC;
          XNOR1 : out STD_LOGIC);
end logic_gates;
architecture Behavioral of logic_gates is
begin
AND1<=A AND B;
OR1<=A OR B;
NOT1<=NOT A;
XOR1<=A XOR B;
NAND1<= A NAND B;
NOR1<=A NOR B;
XNOR1<=A XNOR B;
end Behavioral;
```

## Synthesis Report

### A) Final Report:

Final Results

RTL Top Level Output File Name : logic\_gates.ngr

Top Level Output File Name : logic\_gates

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : NO

### B) Design Statistics

# IOs : 9

**Cell Usage :**

# BELS : 7

# INV : 1

# LUT2 : 6

# IO Buffers : 9

# IBUF : 2

# OBUF : 7

=====

### Device utilization summary:

Selected Device : 3s250eft256-5

Number of Slices: 4 out of 2448 0%

Number of 4 input LUTs: 7 out of 4896 0%

Number of IOs: 9

Number of bonded IOBs: 9 out of 172 5%

### C) TIMING REPORT:

Delay: 5.998ns (Levels of Logic = 3)

Source: A (PAD)

Destination: NOR1 (PAD)

#### Data Path: A to NOR1

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
IBUF:I->O	7	1.106	0.754	A_IBUF (A_IBUF)
LUT2:I0->O	1	0.612	0.357	OR11 (OR1_OBUF)

OBUF:I->O	3.169	OR1_OBUF (OR1)
-----		
Total	5.998ns	

**VHDL Test bench:**

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_unsigned.all;

USE ieee.numeric_std.ALL;

ENTITY tb_logic_gates_vhd IS

END tb_logic_gates_vhd;

ARCHITECTURE behavior OF tb_logic_gates_vhd IS

    COMPONENT logic_gates

    PORT(

        A : IN std_logic;

        B : IN std_logic;

        AND1 : OUT std_logic;

        OR1 : OUT std_logic;

        NOT1 : OUT std_logic;

        XOR1 : OUT std_logic;

        NAND1 : OUT std_logic;

        NOR1 : OUT std_logic;

        XNOR1 : OUT std_logic

    );

END COMPONENT;

SIGNAL A : std_logic := '0';

SIGNAL B : std_logic := '0';

SIGNAL AND1 : std_logic;
```

SIGNAL OR1 : std\_logic;

SIGNAL NOT1 : std\_logic;


SIGNAL XOR1 : std\_logic;

SIGNAL NAND1 : std\_logic;

SIGNAL NOR1 : std\_logic;

SIGNAL XNOR1 : std\_logic;

## Simulation Results:

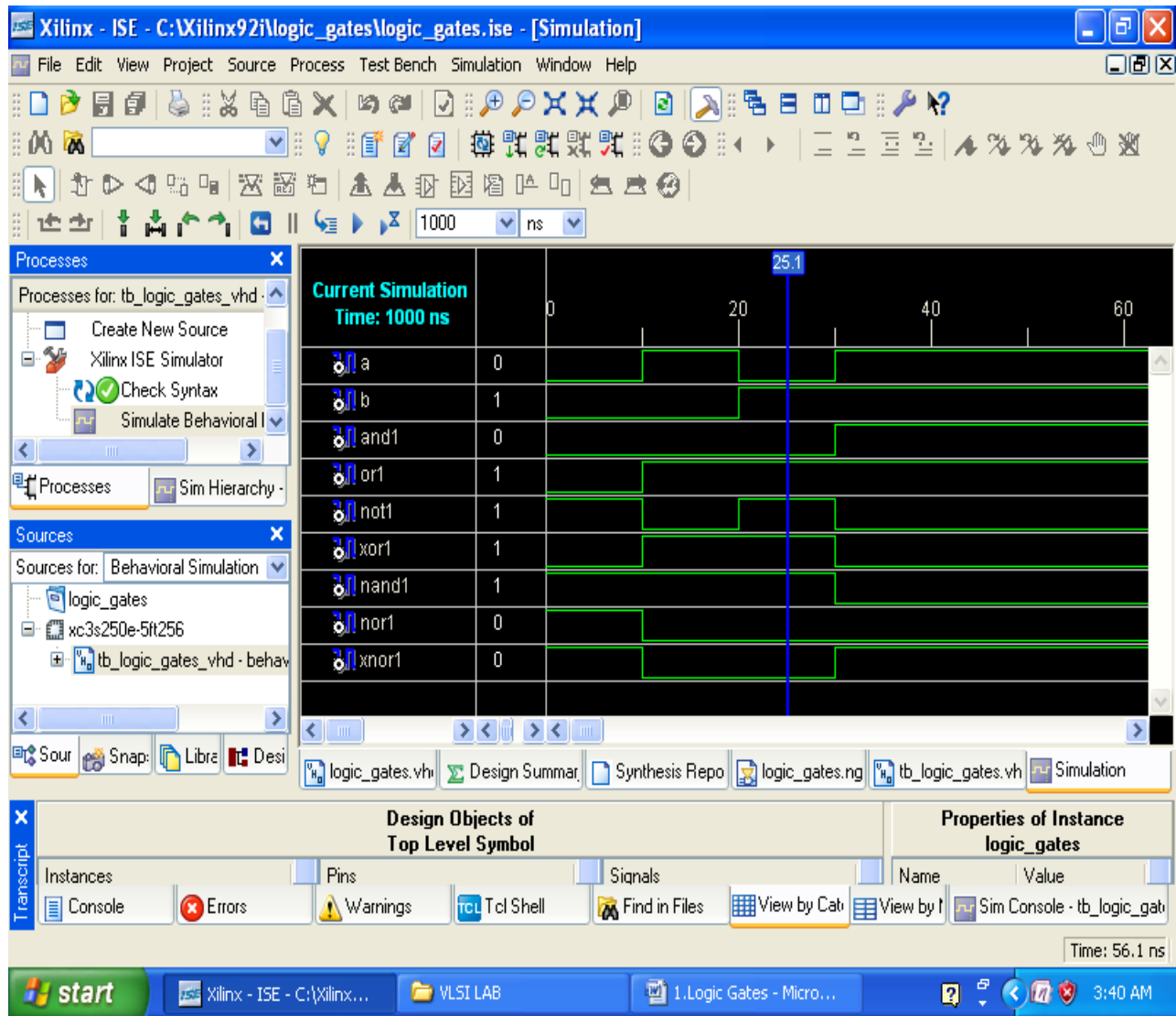

```
BEGIN

    uut: logic_gates PORT MAP(

        A => A,

        B => B,

        AND1 => AND1,

        OR1 => OR1,

        NOT1 => NOT1,

        XOR1 => XOR1,

        NAND1 => NAND1,

        NOR1 => NOR1,

        XNOR1 => XNOR1

    );

    A<='1' AFTER 10NS,'0' AFTER 20NS,'1' AFTER 30NS;


    B<='1' AFTER 20NS;

END;
```

**Result:** Logic Gates are designed using VHDL and simulated the same using Xilinx ISE Simulator

**Schematic Diagram:**



 

**Experiment No:3****8-To-1 Multiplexer**

---

**Aim:** To Design **8-To-1 Multiplexer** using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

**VHDL Code:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity Mux_8_1 is
    Port ( En_L : in STD_LOGIC;
          S : in STD_LOGIC_VECTOR (2 downto 0);
          I : in STD_LOGIC_VECTOR (7 downto 0);
          Y : out STD_LOGIC);
end Mux_8_1;
architecture Behavioral of Mux_8_1 is
begin
    process(S,I,En_L)
    begin
        if En_L='1' then Y<='0';
        else
            case S is
                when "000"=>Y<=I(0);
                when "001"=>Y<=I(1);
                when "010"=>Y<=I(2);
                when "011"=>Y<=I(3);
                when "100"=>Y<=I(4);
                when "101"=>Y<=I(5);
                when "110"=>Y<=I(6);
```

```
when "111"=>Y<=I(7);
```

```
when others=>Y<='Z';
```

```
end case;
```

```
end if;
```

```
end process;
```

```
end Behavioral;
```

## Synthesis Report

### Final Report:

Final Results

RTL Top Level Output File Name : Mux\_8\_1.ngr

Top Level Output File Name : Mux\_8\_1

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : NO

### Design Statistics

# IOs : 13

### Cell Usage :

# BELS : 8

# LUT3 : 1

# LUT4 : 5

# MUXF5 : 2

# IO Buffers : 13

# IBUF : 12

# OBUF : 1

---

### Device utilization summary:

Selected Device : 3s250eft256-5

Number of Slices: 3 out of 2448 0%

Number of 4 input LUTs: 6 out of 4896 0%

Number of IOs: 13

Number of bonded IOBs: 13 out of 172 7%

### **TIMING REPORT:**

Delay: 7.512ns (Levels of Logic = 6)

Source: S<0> (PAD)

Destination: Y (PAD)

**Data Path: S<0> to Y**

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
IBUF:I->O	4	1.106	0.651	S_0_IBUF (S_0_IBUF)
LUT4:I0->O	1	0.612	0.000	Y97_F (N85)
MUXF5:I0->O	2	0.278	0.449	Y97 (Y_map27)
LUT3:I1->O	1	0.612	0.000	Y1241 (N89)
MUXF5:I1->O	1	0.278	0.357	Y124_f5 (Y_OBUF)
OBUF:I->O		3.169		Y_OBUF (Y)
Total		7.512ns		

10

### **VHDL Test bench:**

```

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_unsigned.all;

USE ieee.numeric_std.ALL;

ENTITY tb_Mux_8_1_vhd IS
END tb_Mux_8_1_vhd;

ARCHITECTURE behavior OF tb_Mux_8_1_vhd IS
    COMPONENT Mux_8_1
    PORT(
        En_L : IN std_logic;
        S : IN std_logic_vector(2 downto 0);
        I : IN std_logic_vector(7 downto 0);
        Y : OUT std_logic
    );
    END COMPONENT;

    SIGNAL En_L : std_logic := '0';
    SIGNAL S : std_logic_vector(2 downto 0) := (others=>'0');
    SIGNAL I : std_logic_vector(7 downto 0) := (others=>'0');

```

```
SIGNAL Y : std_logic;
BEGIN
    uut: Mux_8_1 PORT MAP(
        En_L => En_L,
        S => S,
        I => I,
        Y => Y
    );
    En_L<='1' after 80ns;
    I<="10101010" after 10ns;
    S<="001" after 10ns,"010" after 20ns,"011" after 30ns,"100" after 40ns,"101" after 50ns,"110" after 60ns,"111"
    after 70ns;
END;
```

**Result:** 8-To-1 Multiplexer is designed using VHDL and simulated the same using Xilinx ISE Simulator.

11


**Simulation Results:**

**Current Simulation Time: 1000 ns**

Signal	Value	Hex Value
en_1	0	
s[2:0]	3'h4	3'h0, 3'h1, 3'h2, 3'h3, 3'h4, 3'h5, 3'h6, 3'h7
i[7:0]	8'hAA	8'h00, 8'hAA
i[7]	1	
i[6]	0	
i[5]	1	
i[4]	0	
i[3]	1	
i[2]	0	
i[1]	1	
i[0]	0	
y	0	

View the history list of schematics

**Schematic Diagram:**

 **HDL Synthesis Report**

## Macro Statistics

# Xors : 3  
 1-bit xor2 : 3

**Advanced HDL Synthesis Report**

## Macro Statistics

# Xors : 3  
 1-bit xor2 : 3

**Final Report:**

RTL Top Level Output File Name : Binary\_to\_gray.ngc  
 Top Level Output File Name : Binary\_to\_gray  
 Output Format : NGC  
 Optimization Goal : Speed  
 Keep Hierarchy : NO

**Design Statistics**

# IOs : 8

**Cell Usage :**

# BELS : 3  
 # LUT2 : 3  
 # IO Buffers : 8  
 # IBUF : 4  
 # OBUF : 4

**Device utilization summary:****Selected Device : 3s250eft256-5**

Number of Slices: 2 out of 2448 0%  
 Number of 4 input LUTs: 3 out of 4896 0%  
 Number of IOs: 8  
 Number of bonded IOBs: 8 out of 172 4%

**TIMING REPORT:**

Data Path: B<2> to G<2>

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
IBUF:I->O	2	1.106	0.532	B_2_IBUF (B_2_IBUF)
LUT2:I0->O	1	0.612	0.357	Mxor_G<2>_Result1 (G_2_OBUF)
OBUF:I->O		3.169		G_2_OBUF (G<2>)

**Experiment No:4****2-To-4 decoder**

**Aim:** To Design **2-To-4 decoder** using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

**VHDL Code:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity decoder is
    Port ( En : in STD_LOGIC;
          I : in STD_LOGIC_VECTOR (1 downto 0);
          Y : out STD_LOGIC_VECTOR (3 downto 0));
end decoder;
architecture Behavioral of decoder is
begin
    process(En,I)
    begin
        if En='0' then Y<="0000";
        else
            case I is
                when "00" =>Y<="0001";
                when "01" =>Y<="0010";
                when "10" =>Y<="0100";
                when "11" =>Y<="1000";
                when others =>Y<="ZZZZ";
            end case;
        end if;
    end process;
end Behavioral;
```



## Synthesis Report

### Final Report:

#### Final Results

RTL Top Level Output File Name : decoder.ngc  
 Top Level Output File Name : decoder  
 Output Format : NGC  
 Optimization Goal : Speed  
 Keep Hierarchy : NO

#### Design Statistics

# IOs : 7

#### Cell Usage :

# BELS : 4

# LUT3 : 4

# IO Buffers : 7

# IBUF : 3

# OBUF : 4

=====

### Device utilization summary:

Selected Device : 3s250eft256-5

Number of Slices: 2 out of 2448 0%

Number of 4 input LUTs: 4 out of 4896 0%

Number of IOs: 7

Number of bonded IOBs: 7 out of 172 4%

### TIMING REPORT:

Delay: 5.895ns (Levels of Logic = 3)

Source: I<1> (PAD)

Destination: Y<3> (PAD)

Data Path: I<1> to Y<3>

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
IBUF:I->O	4	1.106	0.651	I_1_IBUF (I_1_IBUF)
LUT3:I0->O	1	0.612	0.357	Y<3>1 (Y_3_OBUF)
OBUF:I->O		3.169		Y_3_OBUF (Y<3>)
Total		5.895ns		

**VHDL Test bench:**

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_unsigned.all;

USE ieee.numeric_std.ALL;

ENTITY tb_decoder_vhd IS
END tb_decoder_vhd;


ARCHITECTURE behavior OF tb_decoder_vhd IS
    COMPONENT decoder
    PORT(
        En : IN std_logic;
        I : IN std_logic_vector(1 downto 0);
        Y : OUT std_logic_vector(3 downto 0)
    );
    END COMPONENT;
    SIGNAL En : std_logic := '0';
    SIGNAL I : std_logic_vector(1 downto 0) := (others=>'0');
    SIGNAL Y : std_logic_vector(3 downto 0);


BEGIN
    uut: decoder PORT MAP(
        En => En,
        I => I,
        Y => Y
    );
    En<='1' after 10ns;
    I<="01" after 20ns,"10" after 30ns,"11" after 40ns;

END;
```

**Result:** 2-To-4 Decoder is designed using VHDL and simulated the same using Xilinx ISE Simulator

### Simulation Results:

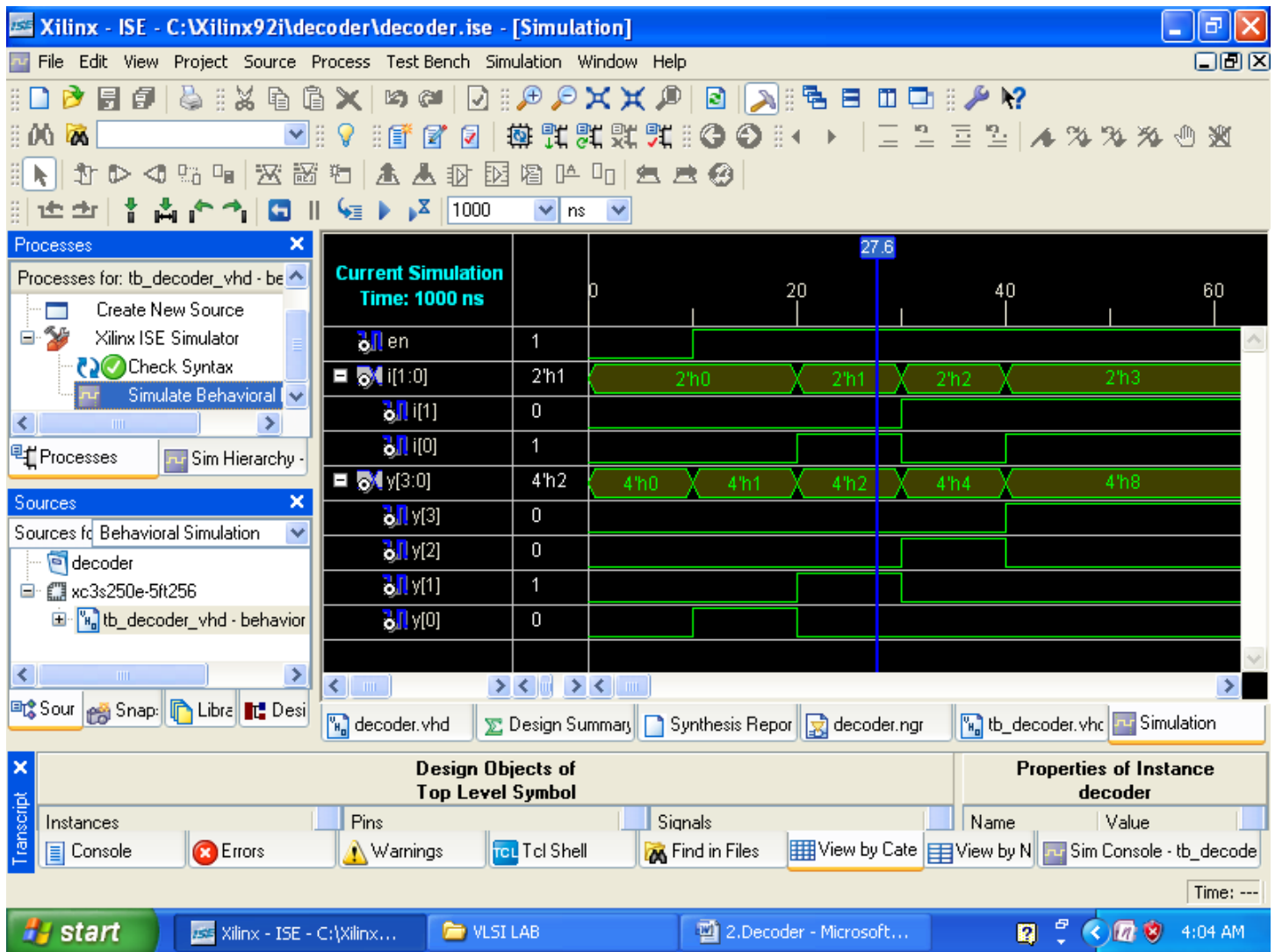

 **Schematic Diagram:****Synthesis Report****Final Report:**

## Final Results

RTL Top Level Output File Name : encoder\_without\_priority.ngr

Top Level Output File Name : encoder\_without\_priority

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : NO

**Design Statistics**

# IOs : 12

**Cell Usage :**

# BELS : 15

# LUT3 : 6

# LUT4 : 9

# IO Buffers : 12

# IBUF : 9

# OBUFT : 3

**Device utilization summary:**

Selected Device : 3s250eft256-5

Number of Slices: 9 out of 2448 0%  
 Number of 4 input LUTs: 15 out of 4896 0%  
 Number of IOs: 12  
 Number of bonded IOBs: 12 out of 172 6%

**TIMING REPORT:**

Delay: 9.315ns (Levels of Logic = 6)

Source: I&lt;0&gt; (PAD)

Destination: Y&lt;2&gt; (PAD)

Data Path: I&lt;0&gt; to Y&lt;2&gt;

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
IBUF:I->O	4	1.106	0.651	I_0_IBUF (I_0_IBUF)
LUT3:I0->O	2	0.612	0.532	Y_mux0000<0>41 (Y_mux0000<0>_bdd4)
LUT3:I0->O	2	0.612	0.449	Y_not0001_inv21 (Y_not0001_inv_bdd3)
LUT4:I1->O	1	0.612	0.509	Y_not0001_inv59 (Y_not0001_inv_map17)
LUT4:I0->O	3	0.612	0.451	Y_not0001_inv93 (Y_not0001_inv)
OBUFT:T->O		3.169		Y_2_OBUFT (Y<2>)

**Experiment No:5(a)****Full Adder Using Dataflow Style**


---

**Aim:** To Design **Full Adder Using Dataflow Style** using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

**VHDL Code:**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity Full_Adder_Dataflow is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          Cin : in STD_LOGIC;
          Sum : out STD_LOGIC;
          Cout : out STD_LOGIC);
end Full_Adder_Dataflow;

```

architecture Dataflow of Full\_Adder\_Dataflow is

signal X: STD\_LOGIC;

begin

X<= (A xor B) and Cin;

Sum<= A xor B xor Cin;

Cout<=X or (A and B);

end Dataflow;

## Synthesis Report

### **HDL Synthesis Report:**

Macro Statistics

# Xors : 2

1-bit xor2 : 2

### **Final Report:**

#### **Final Results**

RTL Top Level Output File Name : Full\_Adder\_Dataflow.ngr

Top Level Output File Name : Full\_Adder\_Dataflow

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : NO

#### **Design Statistics**

# IOs : 5

#### **Cell Usage :**

# BELS : 2

# LUT3 : 2

# IO Buffers : 5

# IBUF : 3

# OBUF : 2

#### **Device utilization summary:**

Selected Device : 3s250eft256-5

Number of Slices: 1 out of 2448 0%  
 Number of 4 input LUTs: 2 out of 4896 0%  
 Number of IOs: 5  
 Number of bonded IOBs: 5 out of 172 2%

**TIMING**

Delay: 5.776ns (Levels of Logic = 3)  
 Source: B (PAD)  
 Destination: Cout (PAD)

**Data Path: B to Cout**

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
IBUF:I->O	2	1.106	0.532	B_IBUF (B_IBUF)
LUT3:I0->O	1	0.612	0.357	Cout1 (Cout_OBUF)
OBUF:I->O		3.169		Cout_OBUF (Cout)
Total		5.776ns		

**VHDL Test bench:**

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;
ENTITY tb_Full_Adder_Dataflow_vhd IS
END tb_Full_Adder_Dataflow_vhd;
ARCHITECTURE behavior OF tb_Full_Adder_Dataflow_vhd IS
    COMPONENT Full_Adder_Dataflow
    PORT(
        A : IN std_logic;
        B : IN std_logic;
  
```

```
Cin : IN std_logic;
Sum : OUT std_logic;
Cout : OUT std_logic
);
END COMPONENT;
SIGNAL A : std_logic := '0';
SIGNAL B : std_logic := '0';
SIGNAL Cin : std_logic := '0';
SIGNAL Sum : std_logic;
SIGNAL Cout : std_logic;
BEGIN
    uut: Full_Adder_Dataflow PORT MAP(
        A => A,
        B => B,
        Cin => Cin,
        Sum => Sum,
        Cout => Cout
    );
    A<='1' after 40ns;
    B<='1' after 20ns,'0' after 40ns,'1'after 60ns;
    Cin<='1' after 10ns,'0' after 20ns,'1' after 30ns,'0' after 40ns,'1' after 50ns, '0' after 60ns,'1' after 70ns;
```

**Result:** Full Adder Using Dataflow Style is designed using VHDL and simulated the same using Xilinx ISE Simulator

### **Simulation Results:**



The screenshot displays the Xilinx ISE simulation environment. The main window shows a timing diagram for a Full Adder simulation. The time axis ranges from 0 to 120 ns, with a vertical cursor at 73.2 ns. The signals being monitored are:


Signal	Value
a	1
b	1
cin	1
sum	1
cout	1

The simulation time is 1000 ns. The interface includes a menu bar (File, Edit, View, Project, Source, Process, Test Bench, Simulation, Window, Help), a toolbar, and several panels:

- Processes:** Shows the simulation process for 'tb\_Full\_Adder\_Dataf'.
- Sources:** Lists the behavioral simulation sources, including 'Full\_Adder\_Dataflow', 'xc3s250e-5ft256', and 'tb\_Full\_Adder\_Dataflow\_vh'.
- Design Objects of Top Level Symbol:** Shows the instance 'Full\_Adder\_Dataflow'.
- Properties of Instance Full\_Adder\_Dataflow:** Displays the instance name and value.

The Windows taskbar at the bottom shows the Start button, 'VLSI LAB' folder, and open windows for 'Xilinx - ISE - C:\Xilinx...', '7(a).Full Adder\_Data...', and the system clock at 2:22 AM.

**Schematic Diagram:**

 

**Experiment No:6****Full Adder Using Behavioral Style**

---

**Aim:** To Design **Full Adder Using Behavioral Style** using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

**VHDL Code:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity Full_Adder_Behavioral is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          Cin : in STD_LOGIC;
          Sum : out STD_LOGIC;
          Cout : out STD_LOGIC);
end Full_Adder_Behavioral;
architecture Behavioral of Full_Adder_Behavioral is
    signal P:Std_logic_vector(2 downto 0);
    begin
        P<=A&B&Cin;
        process(A,B,p,Cin)
        begin
            case p is
                when "000"=>Sum<='0';Cout<='0';
                when "001"=>Sum<='1';Cout<='0';
                when "010"=>Sum<='1';Cout<='0';
                when "011"=>Sum<='0';Cout<='1';
                when "100"=>Sum<='1';Cout<='0';
                when "101"=>Sum<='0';Cout<='1';
                when "110"=>Sum<='0';Cout<='1';
                when "111"=>Sum<='1';Cout<='1';
            end case;
        end process;
    end;
```

```

    when others=>Sum<='Z';Cout<='Z';
  end case;
end process;
end Behavioral;

```

## Synthesis Report

### HDL Synthesis Report

```

Macro Statistics
# ROMs                : 1
8x2-bit ROM           : 1

```

### Final Report:

```

Final Results
RTL Top Level Output File Name  : Full_Adder_Behavioral.ngr
Top Level Output File Name     : Full_Adder_Behavioral
Output Format                   : NGC
Optimization Goal              : Speed
Keep Hierarchy                 : NO

```

### Design Statistics

```
# IOs                : 5
```

### Cell Usage :

```

# BELS                : 2
# LUT3                : 2
# IO Buffers         : 5
# IBUF                : 3
# OBUF                : 2

```

### Device utilization summary:

```

Selected Device : 3s250eft256-5
Number of Slices:      1 out of 2448  0%
Number of 4 input LUTs: 2 out of 4896  0%
Number of IOs:        5
Number of bonded IOBs: 5 out of 172  2%

```

### TIMING REPORT:

```

Delay:      5.776ns (Levels of Logic = 3)
Source:     B (PAD)
Destination: Cout (PAD)

```

Data Path: B to Cout

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
IBUF:I->O	2	1.106	0.532	B_IBUF (B_IBUF)
LUT3:I0->O	1	0.612	0.357	Mrom_P_rom000011 (Mrom_P_rom0000)
OBUF:I->O		3.169		Cout_OBUF (Cout)
Total		5.776ns		

**VHDL Test bench:**

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;
ENTITY tb_Full_Adder_Behavioral_vhd IS
END tb_Full_Adder_Behavioral_vhd;
ARCHITECTURE behavior OF tb_Full_Adder_Behavioral_vhd IS
    COMPONENT Full_Adder_Behavioral
    PORT(
        A : IN std_logic;
        B : IN std_logic;
        Cin : IN std_logic;
        Sum : OUT std_logic;
        Cout : OUT std_logic
    );
    END COMPONENT;
    SIGNAL A : std_logic := '0';
    SIGNAL B : std_logic := '0';
    SIGNAL Cin : std_logic := '0';
    SIGNAL Sum : std_logic;
    SIGNAL Cout : std_logic;
BEGIN
    uut: Full_Adder_Behavioral PORT MAP(
        A => A,
        B => B,
        Cin => Cin,

```

Sum => Sum,

Cout => Cout

);


A<='1' after 40ns;

B<='1' after 20ns,'0' after 40ns,'1'after 60ns;


Cin<='1' after 10ns,'0' after 20ns,'1' after 30ns,'0' after 40ns,'1' after 50ns, '0' after 60ns,'1' after 70ns;

**Result:** Full Adder Using Behavioral Style is designed using VHDL and simulated the same using Xilinx ISE Simulator

### Simulation Results:

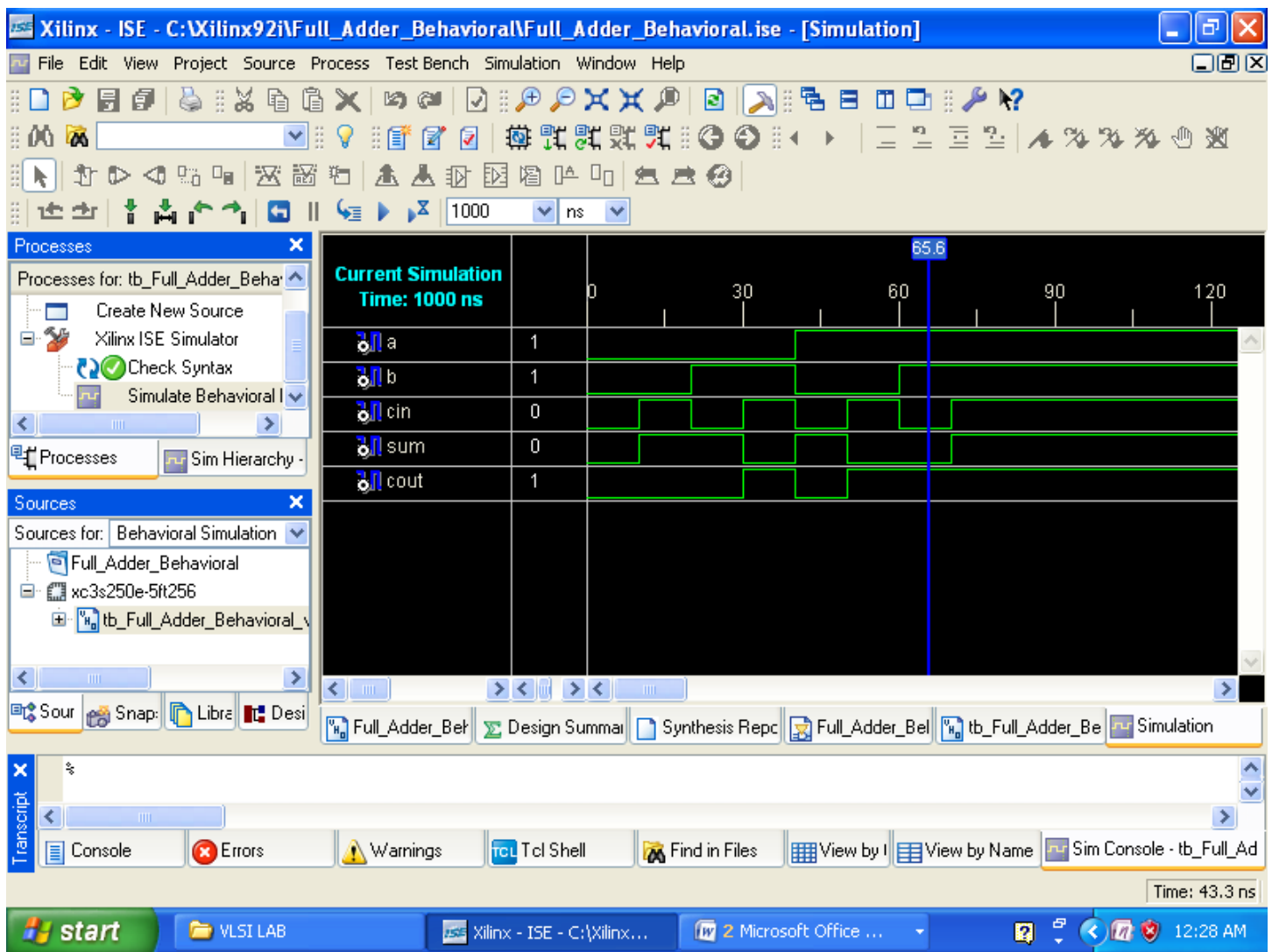

**Schematic Diagram:**

 

## Experiment No:7                      Full Adder Using Structural Style

---

**Aim:** To Design **Full Adder Using Structural Style** using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

### VHDL Code:

```
-----VHDL Code for Xor Gate----  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
entity or_gate is  
    Port ( a : in STD_LOGIC;  
          b : in STD_LOGIC;  
          c : out STD_LOGIC);  
end or_gate;  
architecture Behavioral of or_gate is  
    begin  
        c<=a or b;  
    end Behavioral;  
-----VHDL Code for and Gate-----
```



```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity and_g is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
end and_g;
architecture Behavioral of and_g is
begin
c<=a and b;
end Behavioral;
```

-----VHDL Code for Or Gate-----

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity xor_g is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
end xor_g;
```

```
architecture Behavioral of xor_g is
begin
c<=a xor b;
end Behavioral;
```

-----VHDL Code for Full Adder-----

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity fulladder_structural is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          Cin : in STD_LOGIC;
          SUM : out STD_LOGIC;
          Cout : out STD_LOGIC);
end fulladder_structural;
architecture Behavioral of fulladder_structural is
    component or_gate is
```

```
    port(a,b:in std_logic;
          c:out std_logic);
end component;
component and_g is
    port(a,b:in std_logic;
          c:out std_logic);
end component;
component xor_g is
    port(a,b:in std_logic;
          c:out std_logic);
end component;
    signal y1,y2,y3:std_logic;
begin
x1:xor_g port map(A,B,y1);
a1:and_g port map(A,B,y2);
x2:xor_g port map(y1,Cin,sum);
a2:and_g port map(y1,Cin,y3);
r1:or_gate port map(y2,y3,Cout);
end Behavioral;
```

### **Simulation Results:**

The screenshot displays the Xilinx ISE simulation environment. The main window shows a timing diagram for a full adder circuit. The simulation time is 1000 ns. The diagram plots the signals a, b, cin, sum, and cout over time. A vertical cursor is positioned at 38.7 ns. The signals are as follows:

Signal	Initial Value	Transition Time (ns)
a	0	~38.7
b	1	~10, ~30, ~50, ~70, ~90
cin	1	~10, ~30, ~50, ~70, ~90
sum	0	~10, ~30, ~50, ~70, ~90
cout	1	~10, ~30, ~50, ~70, ~90

The interface includes a menu bar (File, Edit, View, Project, Source, Process, Test Bench, Simulation, Window, Help), a toolbar with various simulation controls, and a status bar at the bottom showing the current time as 4:06 AM. The Windows taskbar at the bottom shows the Start button and open applications including Xilinx ISE and a terminal window titled '7(c).Full Adder\_Struc...'.

**VHDL Test bench:**


```
ENTITY tb_fulladder_structural_vhd IS
END tb_fulladder_structural_vhd;
ARCHITECTURE behavior OF tb_fulladder_structural_vhd IS
    COMPONENT fulladder_structural
    PORT(
        A : IN std_logic;
        B : IN std_logic;
        Cin : IN std_logic;
        SUM : OUT std_logic;
        Cout : OUT std_logic
    );
END COMPONENT;
SIGNAL A : std_logic := '0';
SIGNAL B : std_logic := '0';
SIGNAL Cin : std_logic := '0';
SIGNAL SUM : std_logic;
SIGNAL Cout : std_logic;

BEGIN
    uut: fulladder_structural PORT MAP(
        A => A,
        B => B,
        Cin => Cin,
        SUM => SUM,
        Cout => Cout
    );

    A<='1' after 40ns;
    B<='1' after 20ns,'0' after 40ns,'1'after 60ns;
    Cin<='1' after 10ns,'0' after 20ns,'1' after 30ns,'0' after 40ns,'1' after 50ns, '0' after 60ns,'1' after 70ns;
END;
```

**Result:** Full Adder Using Structural Style is designed using VHDL and simulated the same using Xilinx ISE Simulator

### Schematic Diagram:

 

### Synthesis Report

#### HDL Synthesis Report

##### Macro Statistics

# Registers	: 1
1-bit register	: 1

#### Advanced HDL Synthesis Report

##### Macro Statistics

# Registers	: 1
Flip-Flops	: 1

#### Final Register Report

##### Macro Statistics

# Registers	: 1
Flip-Flops	: 1

#### Final Report:

##### Final Results

RTL Top Level Output File Name	: DFF_Asyn.ngr
Top Level Output File Name	: DFF_Asyn
Output Format	: NGC
Optimization Goal	: Speed

Keep Hierarchy : NO

## Experiment No:8                      8-To-3 Encoder with Priority

---

**Aim:** To Design **8-To-3 Encoder with Priority** using VHDL and simulate the same using Xilinx ISE Simulator.

**Tools Required:** 1.PC

2. Xilinx ISE

**VHDL Code:**


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity Encoder_with_priority is
    Port ( En : in STD_LOGIC;
          I : in STD_LOGIC_VECTOR (7 downto 0);
          Y : out STD_LOGIC_VECTOR (2 downto 0));
end Encoder_with_priority;
architecture Behavioral of Encoder_with_priority is
begin
process(En,I)
begin
    if En='0' then Y<="XXX";
    elsif I(7)='1' then Y<="111";
    elsif I(6)='1' then Y<="110";
    elsif I(5)='1' then Y<="101";
    elsif I(4)='1' then Y<="100";
    elsif I(3)='1' then Y<="011";
    elsif I(2)='1' then Y<="010";
```

```

elseif I(1)='1' then Y<="001";
elseif I(0)='1' then Y<="000";
else Y<="ZZZ";
end if;
end process;
end Behavioral;

```

### Simulation Results:

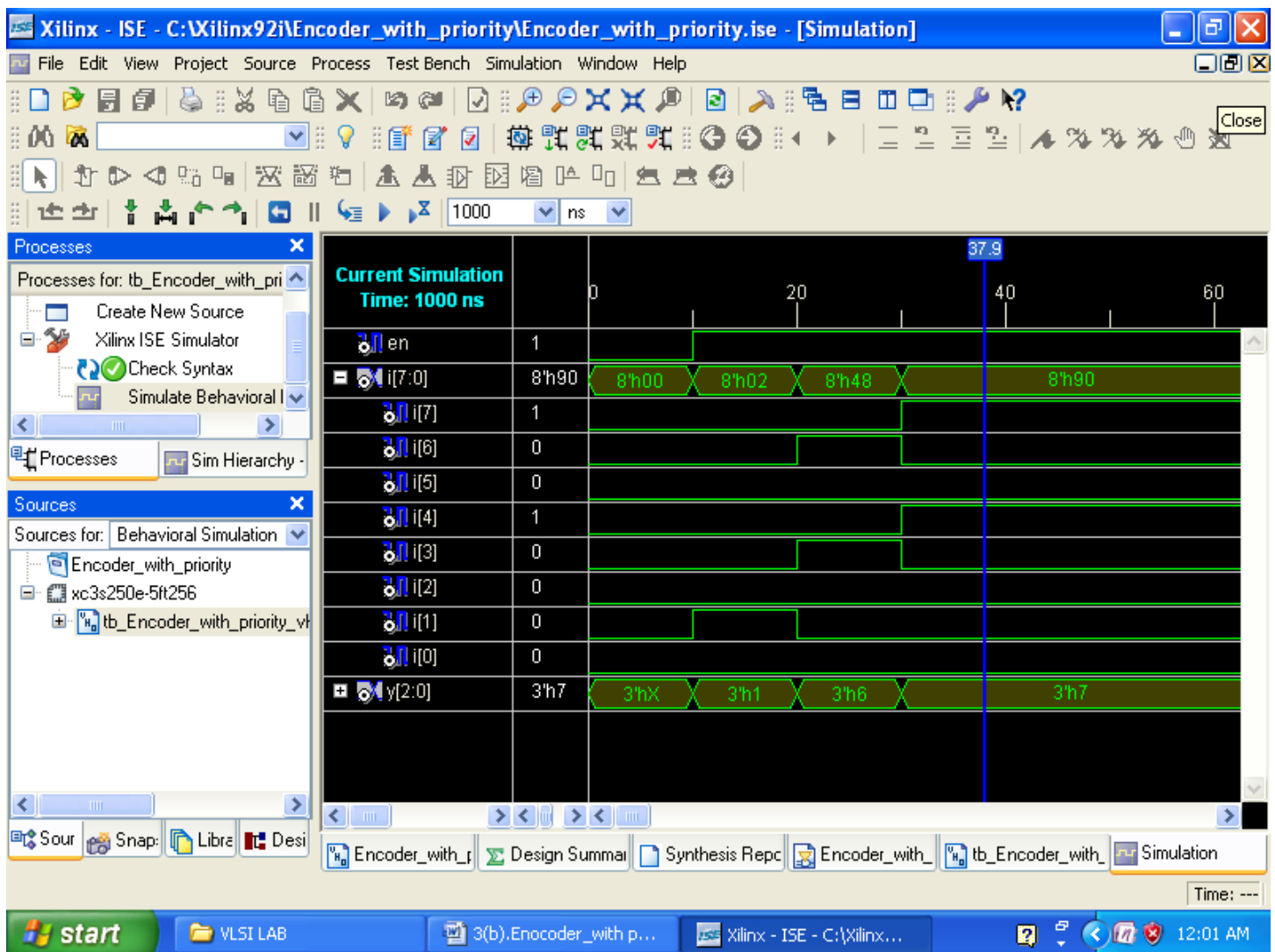

**VHDL Test bench:**

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_unsigned.all;

USE ieee.numeric_std.ALL;

ENTITY tb_encoder_with_priority_vhd IS
END tb_encoder_with_priority_vhd;

ARCHITECTURE behavior OF tb_encoder_with_priority_vhd IS
    COMPONENT encoder_with_priority
    PORT(
        En : IN std_logic;
        I : IN std_logic_vector(7 downto 0);
        Y : OUT std_logic_vector(2 downto 0)
    );
    END COMPONENT;
    SIGNAL En : std_logic := '0';
    SIGNAL I : std_logic_vector(7 downto 0) := (others=>'0');
    SIGNAL Y : std_logic_vector(2 downto 0);


BEGIN
```



```
    uut: encoder_with_priority PORT MAP(  
        En => En,  
        I => I,  
        Y => Y  
    );  
    En<='1' after 10ns;  
    I<="00000010" after 10ns,"00001000" after 20ns,"01000000" after 30ns;
```

**Result:** 8-To-3 Encoder with Priority is designed using VHDL and simulated the same using Xilinx ISE Simulator

### Schematic Diagram:

 

**Experiment No:9****Binary-To-Gray Code Converter**

---

**Aim:** To Design **Binary-To-Gray Code Converter** using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

**VHDL Code:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity Binary_to_gray is
    Port ( B : in  STD_LOGIC_VECTOR (3 downto 0);
          G : out STD_LOGIC_VECTOR (3 downto 0));
end Binary_to_gray;
```

architecture Behavioral of Binary\_to\_gray is

begin

G(3)<=B(3);

G(2)<=B(3) XOR B(2);

G(1)<=B(2) XOR B(1);

G(0)<=B(1) XOR B(0);

end Behavioral;

### **Simulation Results:**

**Xilinx - ISE - C:\Xilinx92i\Binary\_to\_gray\Binary\_to\_gray.ise - [Simulation]**

File Edit View Project Source Process Test Bench Simulation Window Help

1000 ns

**Processes**

Processes for: tb\_Binary\_to\_gray\_v

- Create New Source
- Xilinx ISE Simulator
- Check Syntax
- Simulate Behavioral I

**Sources**

Sources for: Behavioral Simulation

- Binary\_to\_gray
- xc3s250e-5ft256
- tb\_Binary\_to\_gray\_vhd - be

**Current Simulation Time: 1000 ns**

Signal	Initial Value	Value at 13.7 ns
b[3:0]	4'hA	4'h8
b[3]	1	1
b[2]	0	0
b[1]	1	1
b[0]	0	0
g[3:0]	4'hF	4'hC
g[3]	1	1
g[2]	1	1
g[1]	1	1
g[0]	1	1

Time: 35.3 ns

start | Xilinx - ISE - C:\Xilinx... | VLSI LAB | Binary-to Gray - Micr... | 4:50 AM

**VHDL Test bench:**

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_unsigned.all;

USE ieee.numeric_std.ALL;

ENTITY tb_Binary_to_gray_vhd IS
END tb_Binary_to_gray_vhd;


ARCHITECTURE behavior OF tb_Binary_to_gray_vhd IS
    COMPONENT Binary_to_gray
    PORT(
        B : IN std_logic_vector(3 downto 0);
        G : OUT std_logic_vector(3 downto 0)
    );
    END COMPONENT;
    SIGNAL B : std_logic_vector(3 downto 0) := (others=>'0');
    SIGNAL G : std_logic_vector(3 downto 0);

BEGIN
    uut: Binary_to_gray PORT MAP(
        B => B,
        G => G
    );
    B<="1010" after 10ns,"1000" after 20ns;

END;
```

**Result:** Binary-To-Gray Code Converter is designed using VHDL and simulated the same using Xilinx ISE Simulator

### Schematic Diagram:

 

### Synthesis Report

#### HDL Synthesis Report

Macro Statistics

# Comparators : 2  
 4-bit comparator equal : 1  
 4-bit comparator greater : 1

#### Final Report:

RTL Top Level Output File Name : comparator.ngr

Top Level Output File Name : comparator

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : NO

#### Design Statistics

# IOs : 11

#### Cell Usage :

# BELS : 12

# LUT4 : 9

# MUXF5 : 3

# IO Buffers : 11

# IBUF : 8

# OBUF : 3

#### Device utilization summary:

Selected Device: 3s250eft256-5

Number of Slices: 5 out of 2448 0%

Number of 4 input LUTs: 9 out of 4896 0%

Number of IOs: 11

Number of bonded IOBs: 11 out of 172 6%

#### TIMING REPORT:

Data Path: B<1> to AGTB

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
-----				

IBUF:I->O	3	1.106	0.603	B_1_IBUF (B_1_IBUF)
LUT4:I0->O	2	0.612	0.532	AGTB31 (AGTB_bdd2)
LUT4:I0->O	1	0.612	0.000	AGTB111 (N14)
MUXF5:I1->O	1	0.278	0.357	AGTB11_f5 (AGTB_OBUF)
OBUF:I->O		3.169		AGTB_OBUF (AGTB)
-----				
Total		7.269ns		

## Experiment No:10                      D Flip Flop with Asynchronous “Reset”

---

**Aim:** To Design D Flip Flop with Asynchronous “Reset” using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

### VHDL Code:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity DFF_Asyn is
  Port ( clk : in  STD_LOGIC;
        Rst : in  STD_LOGIC;
        D : in  STD_LOGIC;
        Q : out STD_LOGIC);
end DFF_Asyn;
architecture Behavioral of DFF_Asyn is
begin
  process(clk,D,Rst)
  begin
    if Rst='1' then Q<='0';
    elsif clk'event and clk='1' then
      Q<=D;
    end if;
  end process;
end Behavioral;

```

**Design Statistics**

```
# IOs           : 4
Cell Usage :
# FlipFlops/Latches : 1
#   FDC         : 1
# Clock Buffers  : 1
#   BUFGP       : 1
# IO Buffers     : 3
#   IBUF        : 2
#   OBUF        : 1
```

=====

**Device utilization summary:**

Selected Device : 3s250eft256-5

```
Number of Slices:      0 out of 2448  0%
Number of Slice Flip Flops: 1 out of 4896  0%
Number of IOs:        4
Number of bonded IOBs: 4 out of 172  2%
  IOB Flip Flops:     1
Number of GCLKs:      1 out of 24  4%
```

**TIMING REPORT:**

**Clock Information:**

Clock Signal	Clock buffer(FF name)	Load
clk	BUFGP	1

**Asynchronous Control Signals Information:**

-----+-----+-----+



Control Signal	Buffer(FF name)	Load
Rst	IBUF	1

**Timing Summary:**

Speed Grade: -5

Minimum period: No path found

Minimum input arrival time before clock: 1.731ns

Maximum output required time after clock: 4.040ns

Maximum combinational path delay: No path found

**Timing Detail:**-----  
All values displayed in nanoseconds (ns)

=====

Timing constraint: Default OFFSET IN BEFORE for Clock 'clk'

Total number of paths / destination ports: 1 / 1

-----

Offset: 1.731ns (Levels of Logic = 1)

Source: D (PAD)

Destination: Q (FF)

Destination Clock: clk rising

**Data Path: D to Q**

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
IBUF:I->O	1	1.106	0.357	D_IBUF (D_IBUF)
FDC:D		0.268		Q
Total		1.731ns (1.374ns logic, 0.357ns route)		

-----

Timing constraint: Default OFFSET OUT AFTER for Clock 'clk'

Total number of paths / destination ports: 1 / 1

-----

Offset: 4.040ns (Levels of Logic = 1)

Source: Q (FF)

Destination: Q (PAD)

Source Clock: clk rising

**Data Path: Q to Q:**

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
FDC:C->Q	1	0.514	0.357	Q (Q_OBUF)
OBUF:I->O		3.169		Q_OBUF (Q)
Total		4.040ns		

**Simulation Results:**

**Xilinx - ISE - C:\Xilinx92i\DFF\_Asyn\DFF\_Asyn.ise - [Simulation]**

File Edit View Project Source Process Test Bench Simulation Window Help

1000 ns

**Processes**

Processes for: tb\_DFF\_Asyn\_vhd -

- Create New Source
- Xilinx ISE Simulator
- Check Syntax
- Simulate Behavioral

**Sources**

Sources for: Behavioral Simulation

- DFF\_Asyn
- xc3s250e-5ft256
- tb\_DFF\_Asyn\_vhd - behavi

**Current Simulation Time: 1000 ns**

Signal	Initial Value	Value at 42.3 ns
clk	0	1
rst	1	0
d	1	0
q	0	0

**Design Objects of Top Level Symbol**

C:\Xilinx92i\DFF\_Asyn\DFF\_Asyn.ngr

**DFF\_Asyn**

Instances Pins Signals Name Value

Console Errors Warnings Tcl Shell Find in Files View by Cat View by t Sim Console - tb\_DFF\_Asy

Time: ---

start | Xilinx - ISE - C:\Xilinx... | VLSI LAB | D Flip Flop With Asyn ... | 4:25 AM

**VHDL Test bench:**

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_unsigned.all;

USE ieee.numeric_std.ALL;

ENTITY tb_DFF_Asyn_vhd IS

END tb_DFF_Asyn_vhd;

ARCHITECTURE behavior OF tb_DFF_Asyn_vhd IS

    COMPONENT DFF_Asyn

    PORT(clk : IN std_logic;

         Rst : IN std_logic;

         D : IN std_logic;

         Q : OUT std_logic

        );

    END COMPONENT;

    SIGNAL clk : std_logic := '0';

    SIGNAL Rst : std_logic := '0';

    SIGNAL D : std_logic := '0';

    SIGNAL Q : std_logic;

BEGIN

    uut: DFF_Asyn PORT MAP(

        clk => clk,

        Rst => Rst,

        D => D,

        Q => Q );

    Rst<='1' after 40ns;


    clk<= not clk after 10ns;

    D<='1' after 20ns;
```

END;

**Result:** D Flip Flop with Asynchronous "Reset" is designed using VHDL and simulated the same using Xilinx ISE Simulator

**Schematic Diagram:**

 

## Experiment No:11                      D Flip Flop with Synchronous “Reset”

---

**Aim:** To Design D Flip Flop with Synchronous “Reset” using VHDL and simulate the same using Xilinx ISE Simulator


**Tools Required:** 1.PC

2. Xilinx ISE

### VHDL Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity DFF_Syn is
    Port ( clk : in STD_LOGIC;
          Rst : in STD_LOGIC;
          D : in STD_LOGIC;
          Q : out STD_LOGIC);
end DFF_Syn;
architecture Behavioral of DFF_Syn is
begin
    process
    begin
        wait until clk'event and clk='1';
        if Rst='1' then Q<='0';
        elsif clk'event and clk='1' then
            Q<=D;
        end if;
    end process;
end Behavioral;
```

## Simulation Results:

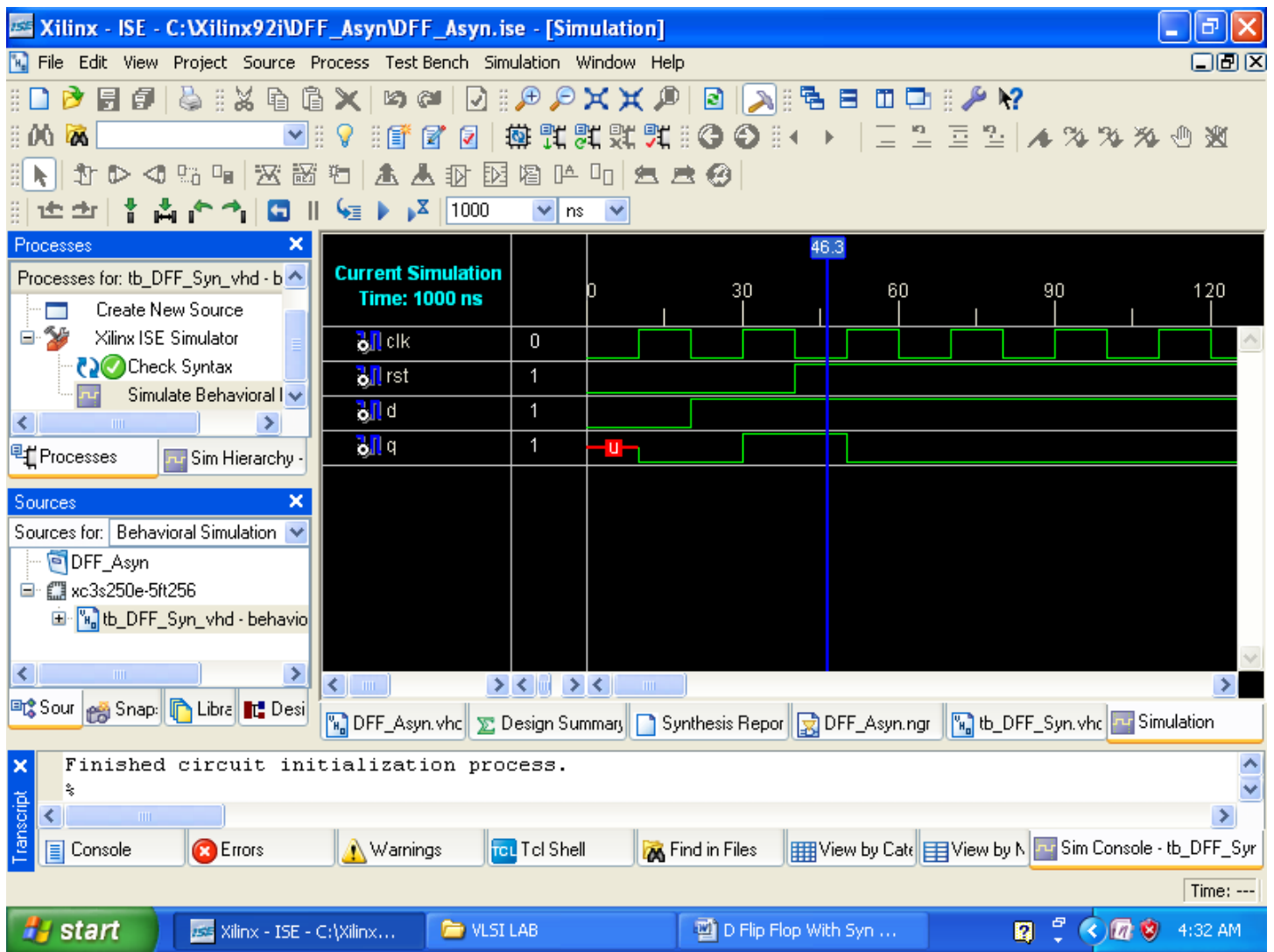

The screenshot displays the Xilinx ISE simulation environment. The main window shows a timing diagram for a D Flip Flop. The signals being monitored are clk, rst, d, and q. The simulation time is 1000 ns. A vertical blue cursor is positioned at 46.3 ns. The q signal shows a transition from 1 to 0 at approximately 15 ns. The console shows the message "Finished circuit initialization process."

**Current Simulation Time: 1000 ns**

Signal	Initial Value	Value at 46.3 ns
clk	0	1
rst	1	1
d	1	1
q	1	0

**Sources:** Behavioral Simulation

- DFF\_Asyn
- xc3s250e-5ft256
- tb\_DFF\_Syn\_vhd - behavior

**Console:** Finished circuit initialization process.

**Taskbar:** Xilinx - ISE - C:\Xilinx... | VLSI LAB | D Flip Flop With Syn ... | 4:32 AM

**VHDL Test bench:**

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.all;
USE ieee.numeric_std.ALL;
ENTITY tb_DFF_Syn_vhd IS
END tb_DFF_Syn_vhd;
ARCHITECTURE behavior OF tb_DFF_Syn_vhd IS
    COMPONENT DFF_Syn
        PORT(clk : IN std_logic;
            Rst : IN std_logic;
            D : IN std_logic;
            Q : OUT std_logic
        );
    END COMPONENT;
    SIGNAL clk : std_logic := '0';
    SIGNAL Rst : std_logic := '0';
    SIGNAL D : std_logic := '0';
```



```
SIGNAL Q : std_logic;

BEGIN

    uut: DFF_Syn PORT MAP(

        clk => clk,

        Rst => Rst,

        D => D,

        Q => Q );

    Rst<='1' after 40ns;

    clk<= not clk after 10ns;

    D<='1' after 20ns;

END;
```

**Result:** D Flip Flop with Synchronous “Reset” is designed using VHDL and simulated the same using Xilinx ISE Simulator

### Schematic Diagram:



### Synthesis Report

#### HDL Synthesis Report

##### Macro Statistics

# Registers : 1

1-bit register : 1

#### Advanced HDL Synthesis Report

##### Macro Statistics

VLSI Lab

# Registers : 1

Flip-Flops : 1

### Final Register Report

#### Macro Statistics

# Registers : 1

Flip-Flops : 1

### Final Report:

#### Final Results

RTL Top Level Output File Name : DFF\_Asyn.ngr

Top Level Output File Name : DFF\_Asyn

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : NO

55

## Experiment No:12 T Flip Flop with Asynchronous “Reset”

---

**Aim:** To Design T Flip Flop with Asynchronous “Reset” using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

### VHDL Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity TFF_Asyn is
    Port ( Rst : in STD_LOGIC;
          clk : in STD_LOGIC;
          T : in STD_LOGIC;
          Q : out STD_LOGIC);
```

```
end TFF_Asyn;
architecture Behavioral of TFF_Asyn is
begin
  process(Rst,Clk,T)
  begin
    if Rst='1' then Q<='0';
    elsif clk'event and Clk='1' then Q<=not T;
    end if;
  end process;
end Behavioral;
```

**Design Statistics**

```
# IOs          : 4
Cell Usage :
# BELS        : 1
# INV         : 1
# FlipFlops/Latches : 1
# FDC         : 1
# Clock Buffers : 1
# BUFGP       : 1
# IO Buffers  : 3
# IBUF        : 2
# OBUF        : 1
```

=====

**Device utilization summary:**

Selected Device : 3s250eft256-5

Number of Slices: 1 out of 2448 0%  
 Number of Slice Flip Flops: 1 out of 4896 0%  
 Number of IOs: 4  
 Number of bonded IOBs: 4 out of 172 2%  
 IOB Flip Flops: 1  
 Number of GCLKs: 1 out of 24 4%

**TIMING REPORT:****Clock Information:**

```

-----+-----+-----+
Clock Signal      | Clock buffer(FF name) | Load |
-----+-----+-----+
clk               | BUFGP                 | 1    |
-----+-----+-----+

```

**Asynchronous Control Signals Information:**

```

-----+-----+-----+
Control Signal    | Buffer(FF name) | Load |
-----+-----+-----+
Rst               | IBUF            | 1    |
-----+-----+-----+

```

**Timing Summary:**

Speed Grade: -5

Minimum period: No path found

Minimum input arrival time before clock: 2.7004ns

Maximum output required time after clock: 4.040ns

Maximum combinational path delay: No path found

**Timing Detail:**-----  
All values displayed in nanoseconds (ns)

=====

Timing constraint: Default OFFSET IN BEFORE for Clock 'clk'

Total number of paths / destination ports: 1 / 1

-----

Offset: 2.700ns (Levels of Logic = 2)

Source: T (PAD)

Destination: Q (FF)

Destination Clock: clk rising

**Data Path: T to Q**

Gate Net

Cell:in->out	fanout	Delay	Delay	Logical Name (Net Name)
IBUF:I->O	1	1.106	0.357	T_IBUF (T_IBUF)
INV:I->O	1	0.612	0.357	Q_not00011_INV_0 (Q_not0001)
FDC:D		0.268		Q
Total		2.700ns		

Timing constraint: Default OFFSET OUT AFTER for Clock 'clk'

Total number of paths / destination ports: 1 / 1

Offset: 4.040ns (Levels of Logic = 1)  
 Source: Q (FF)  
 Destination: Q (PAD)  
 Source Clock: clk rising

#### Data Path: Q to Q

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
FDC:C->Q	1	0.514	0.357	Q (Q_OBUF)
OBUF:I->O		3.169		Q_OBUF (Q)
Total		4.040ns		

### Simulation Results:

The screenshot displays the Xilinx ISE simulation environment. The main window shows a timing diagram for the design 'tb\_TFF\_Asyn.vhd'. The simulation time is 1000 ns. The diagram shows the following signals:

Signal	Value
rst	1
clk	0
t	0
q	0

The diagram also shows a vertical cursor at 46.9 ns. The simulation time is 1000 ns. The diagram shows the following signals:

The screenshot also shows the 'Processes' and 'Sources' panels. The 'Processes' panel shows the simulation process 'Simulate Behavioral I'. The 'Sources' panel shows the sources for the behavioral simulation, including 'TFF\_Asyn', 'xc3s250e-5ft256', 'tb\_TFF\_Asyn\_vhd - behavior', and 'uut - TFF\_Asyn - Behav'. The 'uut - TFF\_Asyn - Behavioral (TFF\_Asyn.vhd)' source is selected.

**VHDL Test bench:**

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_unsigned.all;

USE ieee.numeric_std.ALL;


ENTITY tb_TFF_Asyn_vhd IS
END tb_TFF_Asyn_vhd;

ARCHITECTURE behavior OF tb_TFF_Asyn_vhd IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT TFF_Asyn
    PORT(
        Rst : IN std_logic;
        clk : IN std_logic;
        T : IN std_logic;
        Q : OUT std_logic
    );
    END COMPONENT;
    SIGNAL Rst : std_logic := '0';
    SIGNAL clk : std_logic := '0';
    SIGNAL T : std_logic := '0';
    SIGNAL Q : std_logic;
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: TFF_Asyn PORT MAP(
        Rst => Rst,
        clk => clk,
        T => T,
        Q => Q
    );
    Clk<= not Clk after 10ns;
    Rst<='1' after 40ns;
```

T<='1' after 10ns,'0' after 30ns;

**Result:** T Flip Flop with Asynchronous “Reset” is designed using VHDL and simulated the same using Xilinx ISE Simulator.

### Schematic Diagram:

 



## Experiment No:13                      T Flip Flop with Synchronous “Reset”

---

**Aim:** To Design T Flip Flop with Synchronous “Reset” using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

### VHDL Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity TFF_Syn is
    Port ( Clk : in STD_LOGIC;
          Rst : in STD_LOGIC;
          T : in STD_LOGIC;
          Q : out STD_LOGIC);
end TFF_Syn;
architecture Behavioral of TFF_Syn is
begin
    process
    begin
        wait until clk'event and clk='1';
```

```
if Rst='1' then Q<='0';  
elsif Clk'event and clk='1' then Q<= not T;  
end if;  
end process;  
end Behavioral;
```

**Simulation Results:**

The screenshot displays the Xilinx ISE simulation environment. The main window shows a timing diagram for a behavioral simulation. The simulation time is 1000 ns. The diagram plots four signals: clk, rst, t, and q. The time axis ranges from 0 to 120 ns, with a vertical cursor at 45.0 ns. The signals are as follows:

Signal	Initial Value	Transition
clk	0	Transitions from 0 to 1 at approximately 10 ns, 30 ns, 50 ns, 70 ns, 90 ns, and 110 ns.
rst	1	Transitions from 1 to 0 at approximately 10 ns, 30 ns, 50 ns, 70 ns, 90 ns, and 110 ns.
t	0	Transitions from 0 to 1 at approximately 10 ns, 30 ns, 50 ns, 70 ns, 90 ns, and 110 ns.
q	1	Transitions from 1 to 0 at approximately 10 ns, 30 ns, 50 ns, 70 ns, 90 ns, and 110 ns.

The interface includes a menu bar (File, Edit, View, Project, Source, Process, Test Bench, Simulation, Window, Help), a toolbar, and several panels: Processes, Sources, Design Summary, Console, Errors, Warnings, TCL Tcl Shell, Find in Files, and Sim Console. The Windows taskbar at the bottom shows the Start button, VLSI LAB folder, and open applications including Xilinx ISE and Microsoft Office.

**VHDL Test bench:**

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_unsigned.all;

USE ieee.numeric_std.ALL;

ENTITY tb_TFF_Syn_vhd IS
END tb_TFF_Syn_vhd;

ARCHITECTURE behavior OF tb_TFF_Syn_vhd IS
    COMPONENT TFF_Syn
    PORT(
        Clk : IN std_logic;
        Rst : IN std_logic;
        T : IN std_logic;
        Q : OUT std_logic
    );
    END COMPONENT;
    SIGNAL Clk : std_logic := '0';
    SIGNAL Rst : std_logic := '0';
    SIGNAL T : std_logic := '0';
    SIGNAL Q : std_logic;

BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: TFF_Syn PORT MAP(
        Clk => Clk,
        Rst => Rst,
        T => T,
        Q => Q
    );
    Clk<= not Clk after 10ns;
    Rst<='1' after 40ns;
```

```
T<='1' after 10ns,'0' after 30ns;
```

```
END;
```

64

**Result:** T Flip Flop with Synchronous “Reset” is designed using VHDL and simulated the same using Xilinx ISE Simulator

### Schematic Diagram:



### Synthesis Report

#### HDL Synthesis Report

##### Macro Statistics

```
# Counters           : 1
4-bit up counter     : 1
```

#### Final Register Report

##### Macro Statistics

```
# Registers          : 4
Flip-Flops           : 4
```

#### Final Report:

##### Final Results

```
RTL Top Level Output File Name : BCD_Counter_Asyn.ngr
Top Level Output File Name     : BCD_Counter_Asyn
Output Format                   : NGC
Optimization Goal               : Speed
Keep Hierarchy                  : NO
```

#### Design Statistics

```
# IOs           : 6
```

#### Cell Usage :

```
# BELS           : 4
# INV            : 1
# LUT2           : 1
# LUT3           : 1
```

```

# LUT4           : 1
# FlipFlops/Latches : 4
# FDC           : 4
# Clock Buffers  : 1
# BUFGP         : 1
# IO Buffers     : 5
# IBUF          : 1
# OBUF          : 4

```

65

```
=====
```

## Experiment No:14

## Counter with Asynchronous Reset

**Aim:** To Design **BCD Counter with Asynchronous Reset** using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC

2. Xilinx ISE

### VHDL Code:

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity BCD_Counter_Asyn is
    Port ( Rst : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Count : Buffer STD_LOGIC_VECTOR (3 downto 0));
end BCD_Counter_Asyn;
architecture Behavioral of BCD_Counter_Asyn is
begin
    process(Rst,Clk,Count)
    begin
        if Rst='1' then Count<="0000";
        elsif Clk'event and clk='1' then
            Count<=Count+1;
            if count="1111" then count<="0000";
        end if;
    end process;
end architecture;

```

```

end if;
end process;
end Behavioral;

```

**Device utilization summary:**

Selected Device : 3s250eft256-5

Number of Slices:	2 out of	2448	0%
Number of Slice Flip Flops:	4 out of	4896	0%
Number of 4 input LUTs:	4 out of	4896	0%
Number of IOs:	6		
Number of bonded IOBs:	6 out of	172	3%
Number of GCLKs:	1 out of	24	4%

**TIMING REPORT:****Clock Information:**

Clock Signal	Clock buffer(FF name)	Load
Clk	BUFGP	4

**Asynchronous Control Signals Information:**

Control Signal	Buffer(FF name)	Load
Rst	IBUF	4

**Timing Summary:**

Speed Grade: -5

Minimum period: 2.289ns (Maximum Frequency: 436.862MHz)

Minimum input arrival time before clock: No path found

Maximum output required time after clock: 4.221ns

Timing constraint: Default period analysis for Clock 'Clk'

Clock period: 2.289ns (frequency: 436.862MHz)

Total number of paths / destination ports: 10 / 4

-----  
Delay: 2.289ns (Levels of Logic = 1)

Source: Count\_0 (FF)

Destination: Count\_0 (FF)

Source Clock: Clk rising

Destination Clock: Clk rising

**Data Path: Count\_0 to Count\_0**

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
FDC:C->Q	5	0.514	0.538	Count_0 (Count_0)
INV:I->O	1	0.612	0.357	Mcount_Count_xor<0>11_INV_0 (Mcount_Count)
FDC:D		0.268		Count_0
-----				
Total		2.289ns		



**Timing constraint: Default OFFSET OUT AFTER for Clock 'Clk'**

Total number of paths / destination ports: 4 / 4

-----

Offset: 4.221ns (Levels of Logic = 1)  
 Source: Count\_0 (FF)  
 Destination: Count<0> (PAD)  
 Source Clock: Clk rising

**Data Path: Count\_0 to Count<0>**

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
FDC:C->Q	5	0.514	0.538	Count_0 (Count_0)
OBUF:I->O		3.169		Count_0_OBUF (Count<0>)
Total		4.221ns		

**Simulation Results:**

**Xilinx - ISE - C:\Xilinx92i\BCD\_Counter\_Asyn\BCD\_Counter\_Asyn.ise - [Simulation]**

File Edit View Project Source Process Test Bench Simulation Window Help

1000 ns

**Processes**

- Processes for: tb\_BCD\_Counter\_As
  - Create New Source
  - Xilinx ISE Simulator
  - Check Syntax
  - Simulate Behavioral

**Sources**

- Sources for: Behavioral Simulation
  - BCD\_Counter\_Asyn
  - xc3s250e-5ft256
    - tb\_BCD\_Counter\_Asyn\_vhd

**Simulation Waveform**

Current Simulation Time: 1000 ns

Signal	Initial Value	Value at 365.5 ns
rst	1	1
clk	0	0
count[3:0]	4'h0	4'h0

Design Summary Simulation

Transcript Console Errors Warnings TCL Tcl Shell Find in Files Sim Console - tb\_BCD\_Counter\_Asyn\_vhd

Time: ---

start VLSI LAB Xilinx - ISE - C:\Xilinx... 12:54 AM

**VHDL Test bench:**

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_unsigned.all;


USE ieee.numeric_std.ALL;

ENTITY tb_BCD_Counter_Asyn_vhd IS
END tb_BCD_Counter_Asyn_vhd;

ARCHITECTURE behavior OF tb_BCD_Counter_Asyn_vhd IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT BCD_Counter_Asyn
    PORT(
        Rst : IN std_logic;
        Clk : IN std_logic;
        Count :Buffer std_logic_vector(3 downto 0)
    );
    END COMPONENT;
    --Inputs
    SIGNAL Rst : std_logic := '0';
    SIGNAL Clk : std_logic := '0';
    --Outputs
    SIGNAL Count : std_logic_vector(3 downto 0);
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: BCD_Counter_Asyn PORT MAP(
        Rst => Rst,
        Clk => Clk,
        Count => Count
    );
    Clk<= not clk after 10ns;
    Rst<='1' after 10ns,'0' after 20ns,'1' after 360ns;
END;
```

**Result:** BCD Counter with Asynchronous Reset is designed using VHDL and simulated the same using Xilinx ISE Simulator

**Schematic Diagram:**

 

## Experiment No:15                      BCD Counter with Asynchronous Reset

---

**Aim:** To Design **BCD Counter with Synchronous Reset** using VHDL and simulate the same using Xilinx ISE Simulator

**Tools Required:** 1.PC


2. Xilinx ISE

### VHDL Code:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity BCD_Counter_Syn is
    Port ( Rst : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Count : Buffer STD_LOGIC_VECTOR (3 downto 0));
end BCD_Counter_Syn;
architecture Behavioral of BCD_Counter_Syn is
begin
    process
    begin
        process
        begin
            wait until clk'event and clk='1';
            if Rst='1' then Count<="0000";
            elsif Clk'event and clk='1' then
                Count<=Count+1;
            if count="1111" then count<="0000";
            end if;
            end if;
        end process;
    end process;
end;
```

end process;  
end Behavioral;

**Simulation Results:**

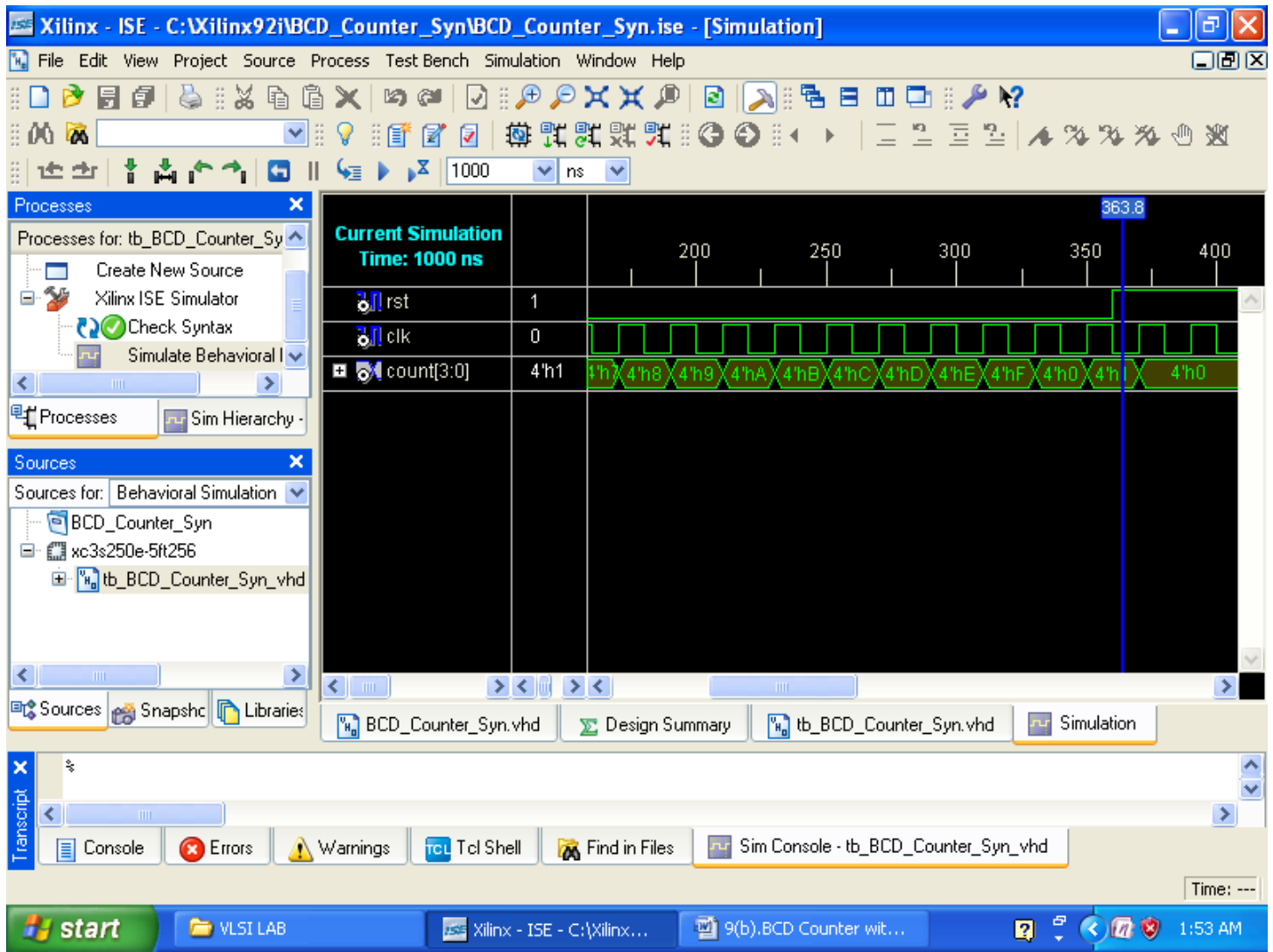

**VHDL Test bench:**

```
LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

USE ieee.std_logic_unsigned.all;

USE ieee.numeric_std.ALL;

ENTITY tb_BCD_Counter_Syn_vhd IS
END tb_BCD_Counter_Syn_vhd;

ARCHITECTURE behavior OF tb_BCD_Counter_Syn_vhd IS
    -- Component Declaration for the Unit Under Test (UUT)
    COMPONENT BCD_Counter_Asyn
    PORT(
        Rst : IN std_logic;
        Clk : IN std_logic;
        Count :Buffer std_logic_vector(3 downto 0)
    );
    END COMPONENT;
    --Inputs
    SIGNAL Rst : std_logic := '0';
    SIGNAL Clk : std_logic := '0';
    --Outputs
    SIGNAL Count : std_logic_vector(3 downto 0);
```

```
BEGIN
    -- Instantiate the Unit Under Test (UUT)
    uut: BCD_Counter_Asyn PORT MAP(
        Rst => Rst,
        Clk => Clk,
        Count => Count
    );
    Clk<= not clk after 10ns;
    Rst<='1' after 10ns,'0' after 20ns,'1' after 360ns;
END;
```

**Result:** BCD Counter with Synchronous Reset is designed using VHDL and simulated the same using Xilinx ISE Simulator