

**Department of**  
**Electrical Engineering**

**LAB MANUAL**  
**ELECTRICAL MACHINES-1**  
**B.Tech-3<sup>rd</sup> Semester**



**KCT College OF ENGG AND  
TECH. VILLAGE FATEHGARH  
DISTT.SANGRUR**

**LIST OF EXPERIMENTS**

1. Open circuit and load characteristics of separately excited DC shunt generators
2. Open circuit and load characteristics of self excited DC shunt generators
3. Load test on d.c. shunt motor
4. Load test on d.c. series motor
5. Load test on d.c.compound motor
6. Speed Control of DC shunt motor.
7. SWINBURNE'S TEST
8. Load test on single-phase transformer
9. Open circuit and short circuit tests on single phase transformer
10. SEPARATION OF NO-LOAD LOSSES IN SINGLE PHASE TRANSFORMER

Ex. No: 1

Date:

**Open circuit and load characteristics of separately excited DC  
shunt generators**

**AIM:**

To obtain open circuit and load characteristics of separately excited DC shunt generator and to find its critical resistance

**APPARATUS REQUIRED:**

Sno	Apparatus	Range	Type	Quantity
1.	Voltmeter	(0-300)V	MC	1
2.	Ammeter	(0-2)A (0-20)A	MC	1
3.	Rheostat	300 $\Omega$ / 1.5 A	-	2
4.	Loading rheostat	20 A	-	1
5.	Three point starter	-	-	1
6.	Connecting wires	-	-	Required

**PRECAUTIONS:**


- Ensure that all the connections are tight.

- The field rheostat of motor should be in minimum resistance position at the time of starting and stopping the machine.
- The field rheostat of generator should be in maximum resistance position at the time of starting and stopping the machine.

### **PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. After checking minimum position of motor field rheostat, maximum position of generator field rheostat,
3. DPST switch is closed and starting resistance is gradually removed.
4. By adjusting the field rheostat, the motor is brought to rated speed.
5. Voltmeter and ammeter readings are taken
6. By varying the generator field rheostat, voltmeter and ammeter readings are taken for OCC characteristics
7. Vary the Generator field rheostat and keep the rated voltage.
8. Load is varied gradually and for each load, voltmeter and ammeter readings are noted for load characteristics.

### **CIRCUIT DIAGRAM:**

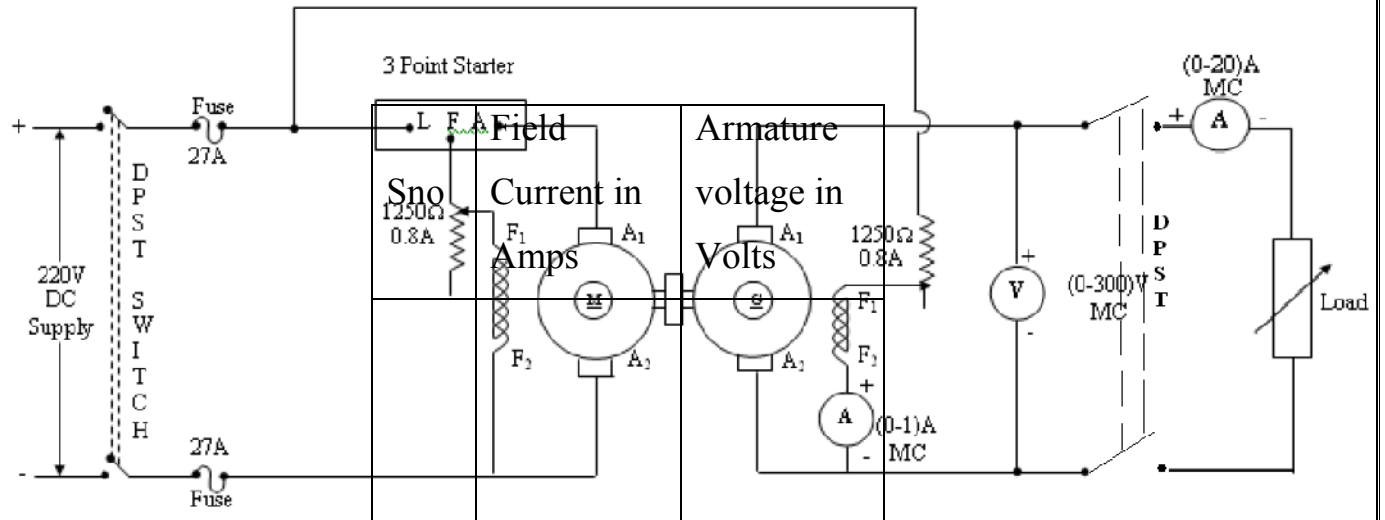

**FUSE RATING:**

125% of rated current  
 $125 \times 21$   
 ----- = A

**NAME PLATE DETAILS:**


**Motor**      **Generator**

Rated Voltage :  
 Rated Current :  
 Rated Power :

**OCC TEST**

**Tabular column:**

**OCC Characteristics:**

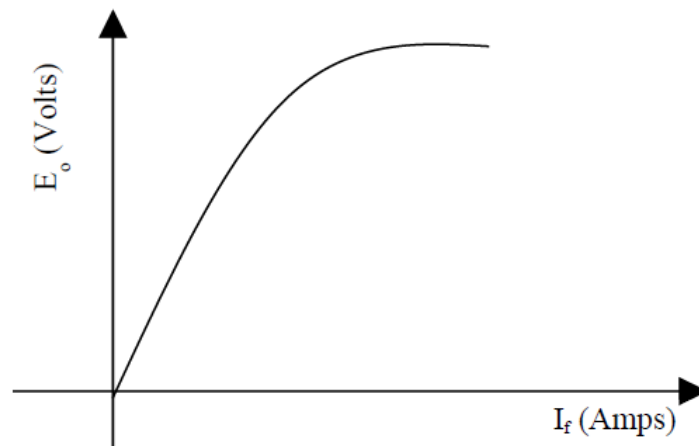


**Load Characteristics:**

$R_a = \text{_____ } \Omega$

**Load Characteristics:**

S.No.	Field Current $I_f$ (Amps)	Load Current $I_L$ (Amps)	Terminal Voltage (V) Volts	$I_a = I_L + I_f$ (Amps)	$E_g = V + I_a R_a$ (Volts)

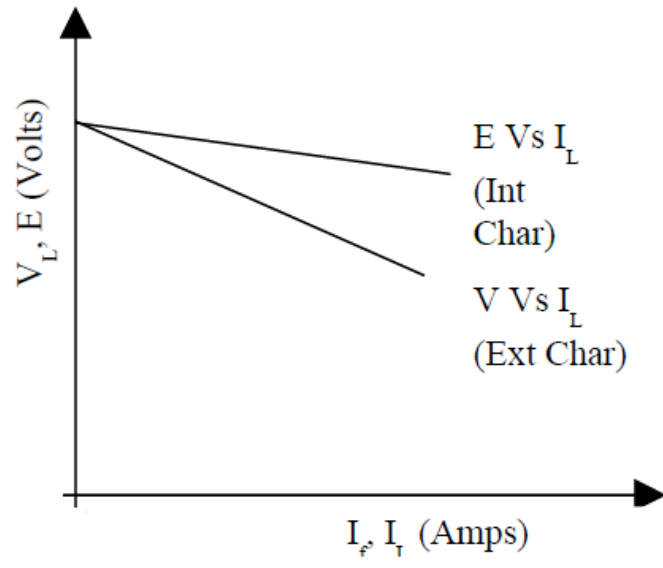

**RESULT:**

Thus the open circuit and load characteristics of separately excited Dc shunt generator is obtained

**Ex. No: 2**

Date:

**Open circuit and load characteristics of self excited DC shunt generators**

**AIM:**

To obtain open circuit and load characteristics of self excited DC shunt generator and to find its critical resistance

**APPARATUS REQUIRED:**

Sno	Apparatus	Range	Type	Quantity
1.	Voltmeter	(0-300)V	MC	1
2.	Ammeter	(0-2)A (0-20)A	MC	1
3.	Rheostat	300 $\Omega$ / 1.5 A	-	2
4.	Loading rheostat	20 A	-	1



5.	Three point starter	-	-	1
6.	Connecting wires	-	-	Required

**PRECAUTIONS:**

- Ensure that all the connections are tight.
- The field rheostat of motor should be in minimum resistance position at the time of starting and stopping the machine.
- The field rheostat of generator should be in maximum resistance position at the time of starting and stopping the machine.

**PROCEDURE:**


1. Connections are made as per the circuit diagram.
2. After checking minimum position of motor field rheostat, maximum position of generator field rheostat,
3. DPST switch is closed and starting resistance is gradually removed.
4. By adjusting the field rheostat, the motor is brought to rated speed.
5. Voltmeter and ammeter readings are taken
6. By varying the generator field rheostat, voltmeter and ammeter readings are taken for OCC characteristics
7. Vary the Generator field rheostat and keep the rated voltage.

8. Load is varied gradually and for each load, voltmeter and ammeter readings are noted for load characteristics.

Sno	Field Current in Amps	Armature voltage in Volts
-----	-----------------------	---------------------------

**CIRCUIT**

**DIAGRAM:**

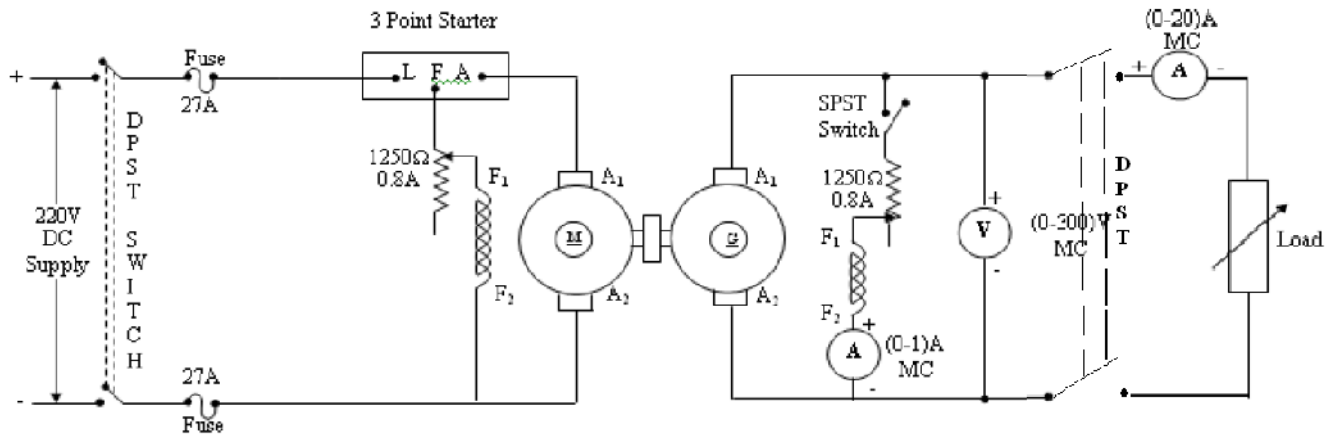

**FUSE RATING:**

125% of rated current

$$\frac{125 \times}{100} = \text{A}$$

**NAME PLATE DETAILS:**

**Motor**

**Generator**


- Rated Voltage :
- Rated Current :
- Rated Power :
- Rated Speed :

**OCC TEST**

**Tabular column:**

--	--	--


**OCC Characteristics:**

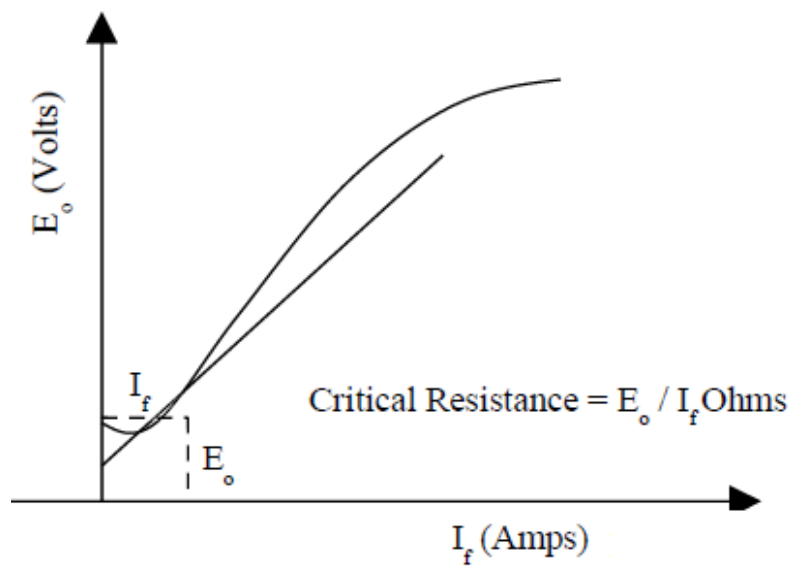

S.No.	Field Current $I_f$ (Amps)	Load Current $I_L$ (Amps)	Terminal Voltage (V) Volts	$I_a = I_L + I_f$ (Amps)	$E_g = V + I_a R_a$ (Volts)

**Load Characteristics:**

$$R_a = \text{_____ } \Omega$$

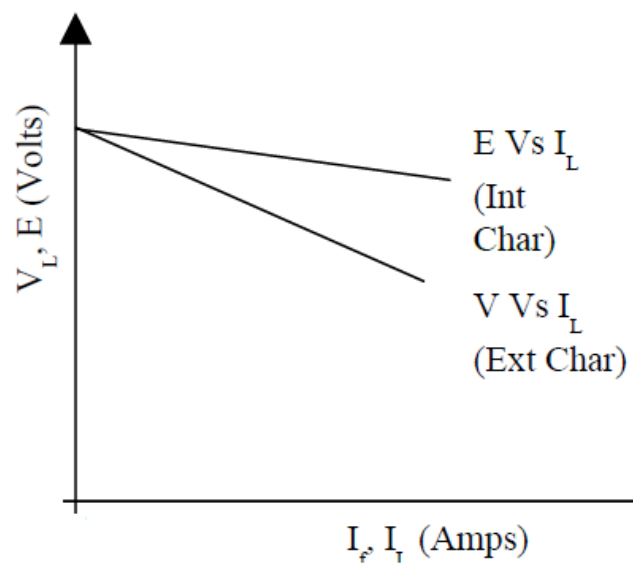**Load Characteristics:**

**RESULT:**

Thus the open circuit and load characteristics of self excited Dc shunt generator is obtained

Ex. No: 3

Date:

**LOAD TEST ON D.C. SHUNT MOTOR****AIM:**

To conduct load test on DC shunt motor and to find efficiency

**Apparatus required:**

Sno	Apparatus	Range	Type	Quantity
1.	Voltmeter	(0-300)V	MC	1
2.	Ammeter	(0-20)A	MC	1
3.	Rheostat	300 $\Omega$ / 1.5 A	-	2
4.	Tachometer	(0-1500) rpm	Digital	1
5.	Connecting wires	-	-	Required

**PRECAUTIONS:**

- Ensure that all the connections are tight.
- DC shunt motor should be started and stopped under no load condition.
- Field rheostat should be kept in the minimum position.
- Brake drum should be cooled with water when it is under load..

**PROCEDURE:**


1. Connections are made as per the circuit diagram
2. After checking the no load condition, and minimum field rheostat position, DPST switch is closed and starter resistance is gradually removed.
3. The motor is brought to its rated speed by adjusting the field rheostat.
4. Ammeter, Voltmeter readings, speed and spring balance readings are noted under no load condition.
5. The load is then added to the motor gradually and for each load, voltmeter, ammeter, spring balance readings and speed of the motor are noted.
6. The motor is then brought to no load condition and field rheostat to minimum position, then DPST switch is opened

**CIRCUITDIAGRAM**



--	--	--	--	--	--	--	--	--	--

**Model graph:**

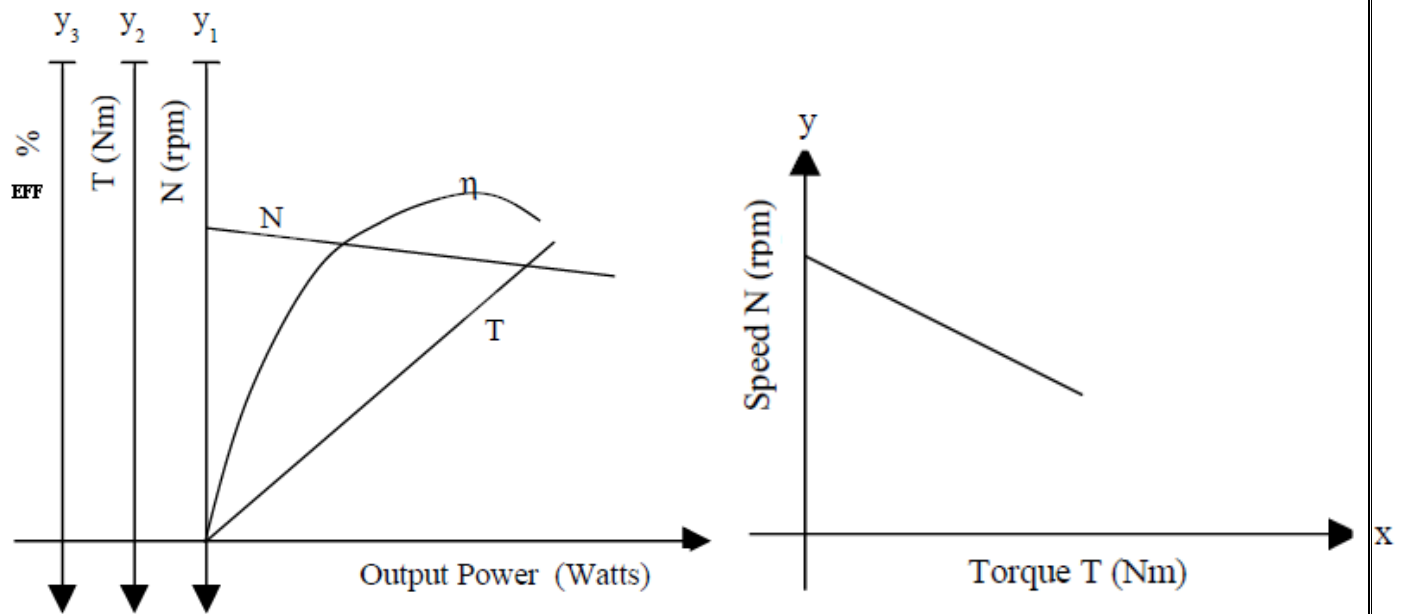

**Model Calculation:**



Circumference of the Brake drum = \_\_\_\_\_ cm

$$R = \frac{\text{circumference}}{2\pi} \text{ metre}$$

$$\text{Torque} = (S1 \sim S2) \times R \times 9.81 \text{ Nm}$$

Input Power  $P_i = V \times I$  Watts

$$\text{Output power} = \frac{2\pi NT}{60} \text{ Watts}$$

$$\text{Efficiency } \eta = \frac{\text{output power}}{\text{input power}} \%$$

**Result:**

Thus load test on DC shunt motor is conducted and its efficiency is determined.

Ex. No: 4

Date:

**LOAD TEST ON D.C.SERIES MOTOR****AIM:**

To conduct load test on DC Series Motor and to find efficiency

**Apparatus required:**

Sno	Apparatus	Range	Type	Quantity
1.	Voltmeter	(0-300)V	MC	1
2.	Ammeter	(0-20)A	MC	1
3.	Tachometer	(0-1500) rpm	Digital	1
4.	Connecting wires	-	-	Required


**PRECAUTIONS:**

- Ensure that all the connections are tight.
- The motor should be started and stopped with load
- Brake drum should be cooled with water when it is under load.

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. After checking the load condition, DPST switch is closed and starter resistance is gradually removed.
3. For various loads, Voltmeter, Ammeter readings, speed and spring balance readings are noted.
4. After bringing the load to initial position, DPST switch is opened.

### CIRCUIT DIAGRAM:

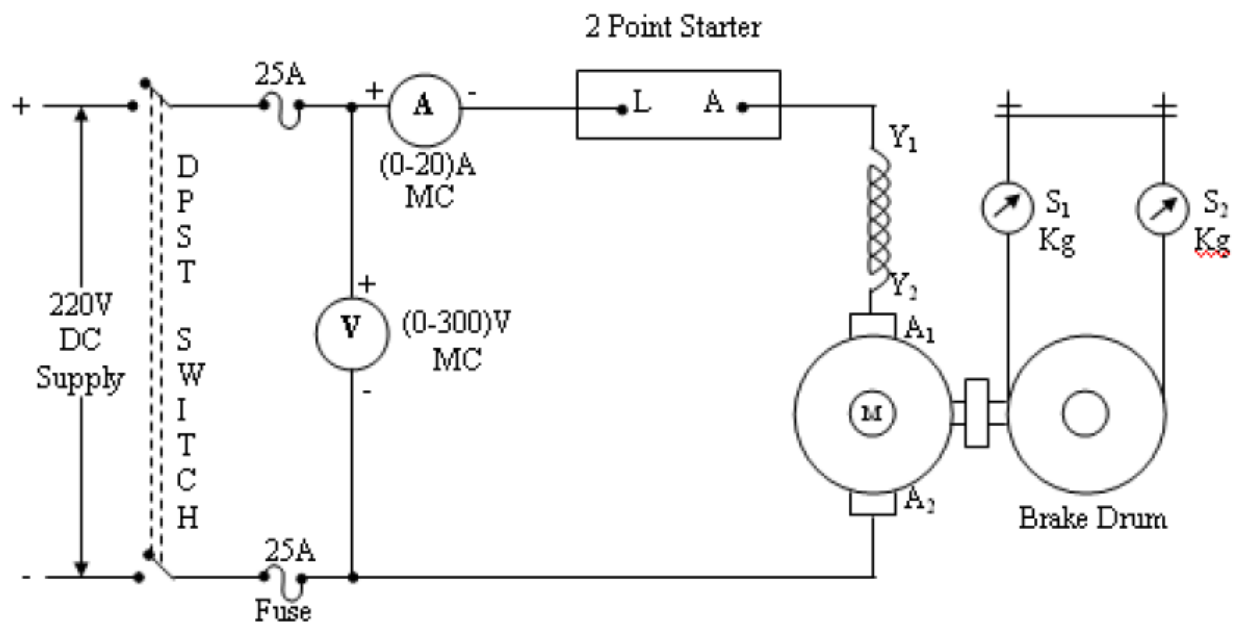

#### FUSE RATING:

125% of rated current

$$\frac{125 \lambda}{100} = \text{A}$$

#### NAME PLATE DETAILS:


Rated Voltage :

Rated Current :

Rated Power :

Rated Speed :

**Model graph:**

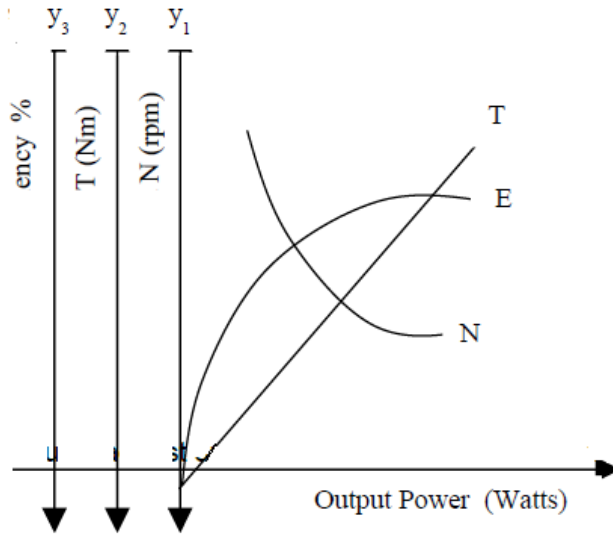

**Tabular Column:**

SNO	Voltage In Volts	Current In Amps	LOAD		Torque T (Nm)	Speed N rpm	Input P <sub>i</sub> watts	Output P <sub>o</sub> watts	Efficiency η in %
			S <sub>1</sub> Kg	S <sub>2</sub> Kg					

**Model calculation:**

Circumference of the Brake drum = \_\_\_\_\_ cm

$$R = \frac{\text{circumference}}{2\pi} \text{ metre}$$

$$\text{Torque} = (S1 \sim S2) \times R \times 9.81 \text{ Nm}$$

$$\text{Input Power } P_i = V \times I \text{ Watts}$$

$$\text{Output power} = \frac{2\pi NT}{60} \text{ Watts}$$

$$\text{Efficiency } \eta = \frac{\text{output power}}{\text{input power}} \%$$

### RESULT:

Thus load test on DC series motor is conducted and its efficiency is determined

Ex. No: 5

Date:

### LOAD TEST ON D.C.COMPOUND MOTOR

#### AIM:

To conduct load test on DC compound motor and to find its efficiency

#### Apparatus required:

Sno	Apparatus	Range	Type	Quantity
1.	Voltmeter	(0-300)V	MC	1

2.	Ammeter	(0-20)A	MC	1
3.	Tachometer	(0-1500) rpm	Digital	1
4.	Rheostat	300 $\Omega$ / 1.5 Amps	-	1
4.	Connecting wires	-	-	Required

**PRECAUTIONS:**

- Ensure that all the connections are tight.
- DC compound motor should be started and stopped under no load condition.
- Field rheostat should be kept in the minimum position.
- Brake drum should be cooled with water when it is under load.

**PROCEDURE:**


1. Connections are made as per the circuit diagram.
2. After checking the no load condition, and minimum field rheostat position, DPST switch is closed and starter resistance is gradually removed.
3. The motor is brought to its rated speed by adjusting the field rheostat.
4. Ammeter, Voltmeter readings, speed and spring balance readings are noted under no load condition.
5. The load is then added to the motor gradually and for each load, voltmeter, ammeter, spring balance readings and speed of the motor are noted.
6. The motor is then brought to no load condition and field rheostat to minimum position, then DPST switch is opened.

**CIRCUIT DIAGRAM**



			Kg	Kg					

**Model graph:**

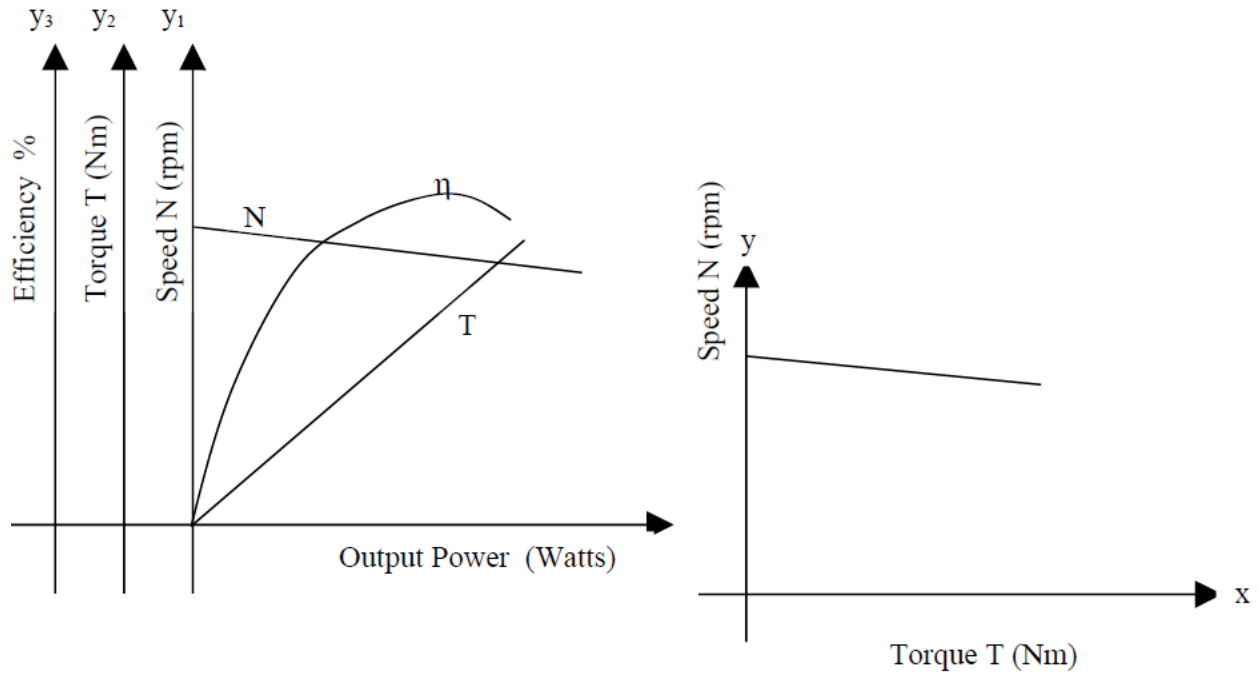



**Model calculations:**

Circumference of the Brake drum = \_\_\_\_\_ cm

$$R = \frac{\text{circumference}}{2\pi} \text{ metre}$$

$$\text{Torque} = (S1 \sim S2) \times R \times 9.81 \text{ Nm}$$

Input Power  $P_i = V \times I$  Watts

$$\text{Output power} = \frac{2\pi NT}{60} \text{ Watts}$$

$$\text{Efficiency } \eta = \frac{\text{output power}}{\text{input power}} \%$$

**RESULT:**

Thus load test on DC Compound Motor is conducted and its efficiency is determined.

Ex. No: 6

Date:

**Speed Control of DC shunt motor.****AIM:**

To obtain speed control of DC shunt motor by

- Varying armature voltage with field current constant.
- Varying field current with armature voltage constant

**Apparatus required:**

Sno	Apparatus	Range	Type	Quantity
1.	Voltmeter	(0-300)V	MC	1
2.	Ammeter	(0-10)A	MC	1
3.	Tachometer	(0-1500) rpm	Digital	1
4.	Rheostat	300 $\Omega$ / 1.5 A 50 $\Omega$ / 5 A	-	1
5.	Connecting wires	-	-	Required

**PRECAUTIONS:**

- Ensure that all the connections are tight.
- Field Rheostat should be kept in the minimum resistance position at the time of starting and stopping the motor.
- Armature Rheostat should be kept in the maximum resistance position at the time of starting and stopping the motor.

**PROCEDURE:**

1. Connections are made as per the circuit diagram.
2. After checking the maximum position of armature rheostat and minimum position of field rheostat, DPST switch is closed


**Armature Control:**

1. Field current is fixed to various values and for each fixed value, by varying the armature rheostat, speed is noted for various voltages across the armature.

**Field Control:**

1. Armature voltage is fixed to various values and for each fixed value, by adjusting the field rheostat, speed is noted for various field currents.
2. Bringing field rheostat to minimum position and armature rheostat to maximum position DPST switch is opened.

**CIRCUIT DIAGRAM**

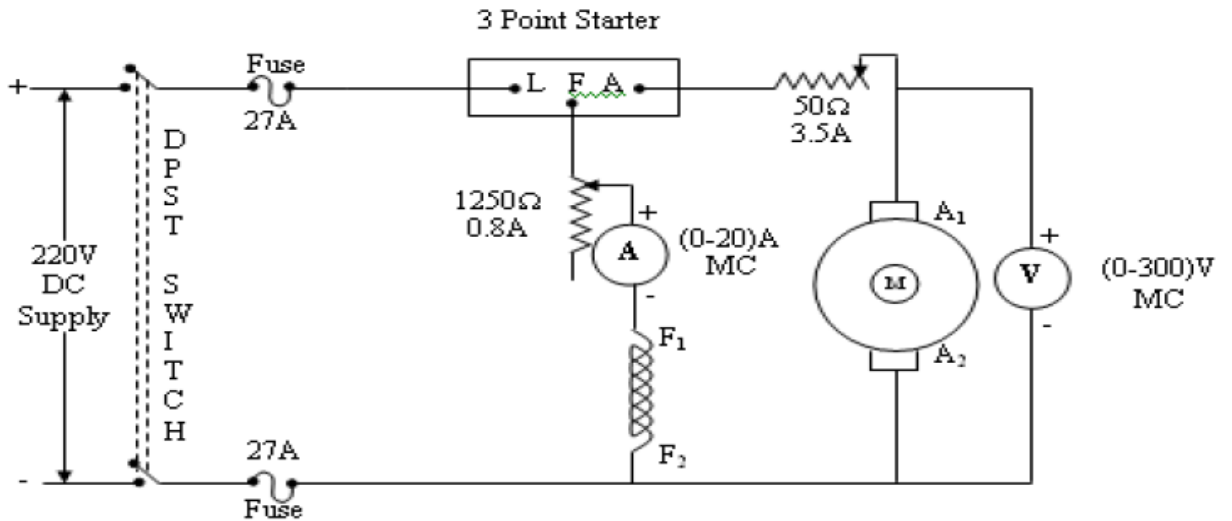

**FUSE RATING:**

125% of rated current

$$\frac{125 \times}{100} = \text{A}$$

**NAME PLATE DETAILS:**

- Rated Voltage :
- Rated Current :
- Rated Power :
- Rated Speed :

**Tabular column:**

**Armature Control Method**

S.no	$I_{f1} =$		$I_{f2} =$		$I_{f3} =$	
	Armature Voltage (V)	Speed N in rpm	Armature Voltage (V)	Speed N in rpm	Armature Voltage (V)	Speed N in rpm


--	--	--	--	--	--	--

### Field Control Method


S.no	$V_{a1} =$		$V_{a2} =$		$V_{a3} =$	
	Field Current in Amps	Speed N in rpm	Field Current in Amps	Speed N in rpm	Field Current in Amps	Speed N in rpm

### Model Graph:

### Armature Control Method

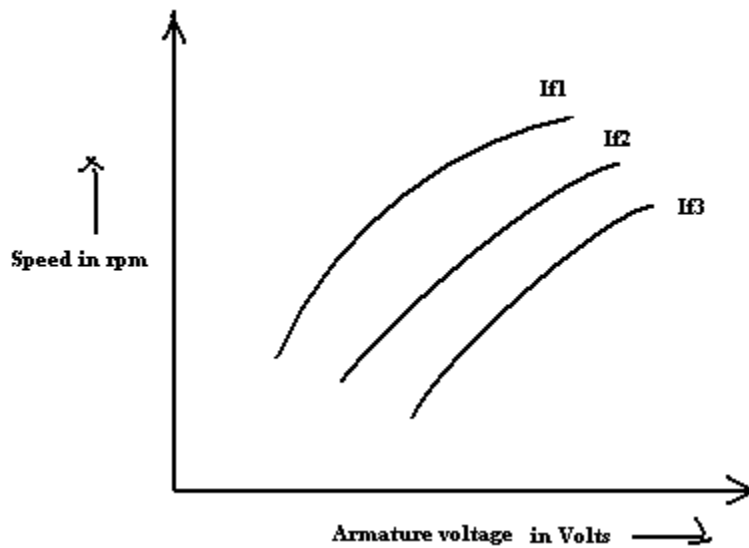

### Field Control Method:

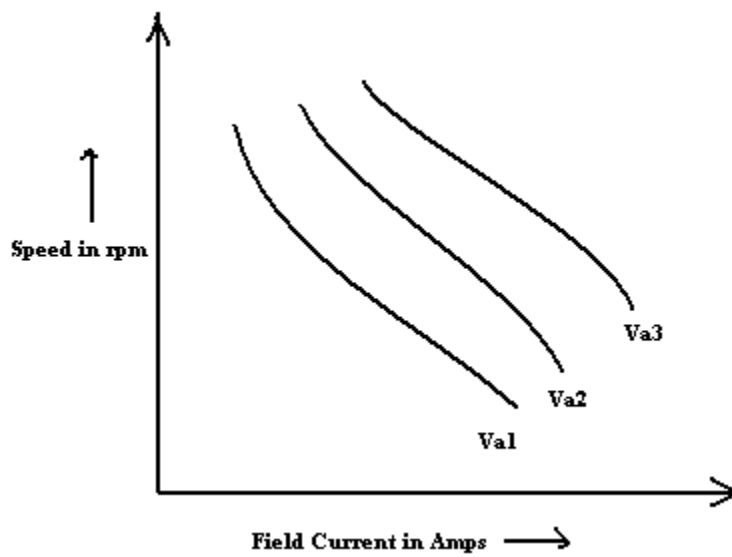

### RESULT:

Thus the speed of the DC shunt motor is controlled by Armature control method and field control method.

Ex. No: 7

Date:

### SWINBURNE'S TEST

#### AIM:

To conduct Swinburne's test on DC machine to determine efficiency when working as generator and motor without actually loading the machine.

#### Apparatus required:

S.no	Apparatus	Range	Type	Quantity
1.	Voltmeter	(0-300)V	MC	1
2.	Ammeter	(0-20)A	MC	1
3.	Tachometer	(0-1500) rpm	Digital	1
4.	Rheostat	300 $\Omega$ / 1.5 A	-	1
5.	Connecting wires	-	-	Required


#### PRECAUTIONS:

- Ensure that all the connections are tight.
- The field rheostat should be in the minimum position at the time of starting and stopping the motor.

#### PROCEDURE:

1. Connections are made as per the circuit diagram.
2. Supply is given by closing the DPST switch.
3. Readings of Ammeter and Voltmeter are noted.
4. Armature resistance in Ohms is calculated as  $R_a = (V \times 1.5) / I$

### CIRCUIT DIAGRAM

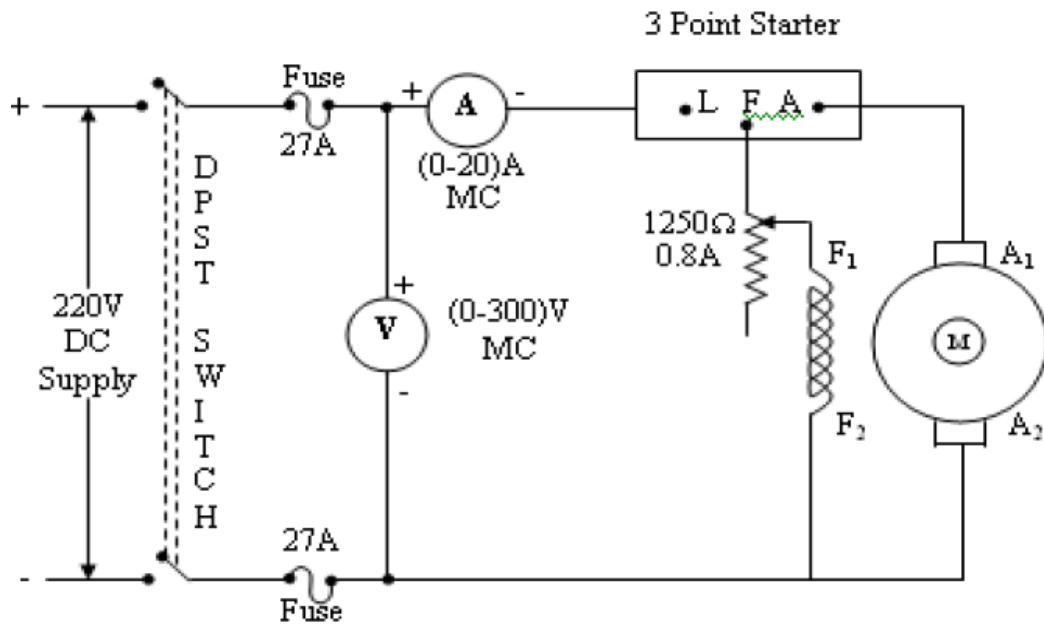

#### FUSE RATING:

125% of rated current

$$\frac{125 \times \text{---}}{100} = \text{---} \text{ A}$$

#### NAME PLATE DETAILS:

Rated Voltage :

Rated Current :

Rated Power :

Rated Speed :

**Tabular column:**




**As a Motor**

SN O	$V_L$ in Volts	$I_L$ in Amps	$I_a$ in Amps	$I_a^2 R_a$ in watts	Total losses in watts	Output Power in watts	Input Power in watts	Efficiency $\eta$ %

**As a Generator**

SN O	$V_L$ in Volts	$I_L$ in Amps	$I_a$ in Amps	$I_a^2 R_a$ in watts	Total losses in watts	Output Power in watts	Input Power in watts	Efficiency $\eta$ %

**Model Graph:**

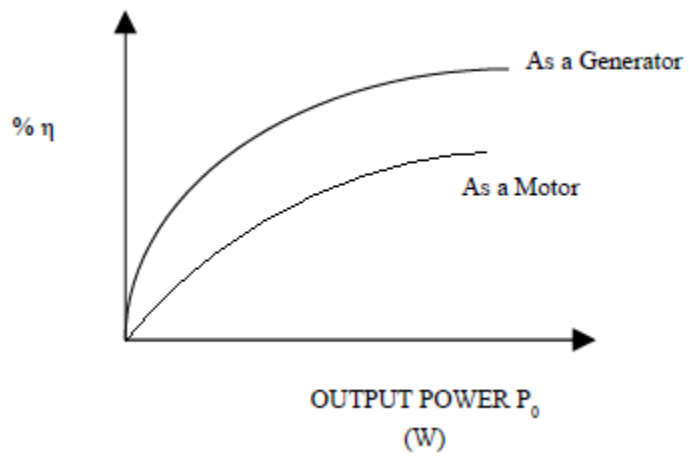

**Model Calculation:**

$$\text{Hot Resistance } R_a = 1.2 \times R \Omega$$

$$\text{Constant losses} = V I_0 - I_{a0}^2 R_a \text{ watts}$$

$$\text{Where } I_{a0} = (I_0 - I_f) \text{ Amps}$$

**AS MOTOR:**

$$\text{Load Current } I_L = \text{_____ Amps (Assume 15\%, 25\%, 50\%, 75\% of rated current)}$$

$$\text{Armature current } I_a = I_L - I_f \text{ Amps}$$

$$\text{Copper loss} = I_a^2 R_a \text{ watts}$$

$$\text{Total losses} = \text{Copper loss} + \text{Constant losses}$$

$$\text{Input Power} = V I_L \text{ watts}$$

$$\text{Output Power} = \text{Input Power} - \text{Total losses}$$

$$\text{Efficiency } \eta \% = \frac{\text{Output power}}{\text{Input Power}} \times 100\%$$

**AS GENERATOR:**

$$\text{Load Current } I_L = \text{_____ Amps (Assume 15\%, 25\%, 50\%, 75\% of rated current)}$$

$$\text{Armature current } I_a = I_L + I_f \text{ Amps}$$

$$\text{Copper loss} = I_a^2 R_a \text{ watts}$$

$$\text{Total losses} = \text{Copper loss} + \text{Constant losses}$$

$$\text{Output Power} = V I_L \text{ watts}$$

$$\text{Input Power} = \text{Input Power} + \text{Total losses}$$

$$\text{Efficiency } \eta \% = \frac{\text{Output power}}{\text{Input Power}} \times 100\%$$

**RESULT:**

Thus the efficiency of DC machine is predetermined by Swinburne's test.



Ex. No: 8

Date:

**Load test on single-phase transformer****AIM:**

To conduct load test on single phase transformer and to find efficiency and percentage regulation

**Apparatus required:**

Sno	Apparatus	Range	Type	Quantity
1.	Voltmeter	(0-300)V	MI	1
		(0-150)V	MI	1
2.	Ammeter	(0-10)A	MI	1
		(0-5)A		1
3.	Wattmeter	300 V, 5 A 150 V, 10 A	UPF	1
4.	1 $\Phi$ Auto Transformer	(0-300) V	-	1
5.	Loading Rheostat	-	-	1
6.	Connecting wires	-	-	Required


**PRECAUTIONS:**

- Ensure that all the connections are tight.
- Auto Transformer should be in minimum position.
- The AC supply is given and removed from the transformer under no load condition.

**PROCEDURE:**

1. Connections are made as per the circuit diagram
2. After checking the no load condition, minimum position of auto transformer and DPST switch is closed.
3. Ammeter, Voltmeter and Wattmeter readings on both primary side and secondary side are noted.
4. The load is increased and for each load, Voltmeter, Ammeter and Wattmeter readings on both primary and secondary sides are noted.
5. Again no load condition is obtained and DPST switch is opened.

**CIRCUIT DIAGRAM:**

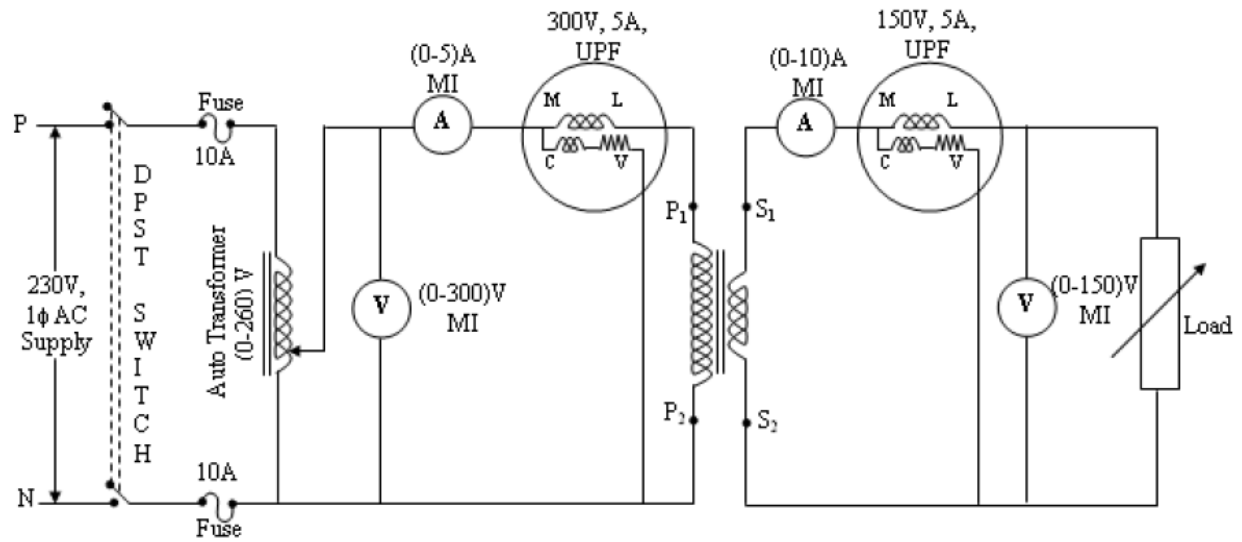

**FUSE RATING:**

125% of rated current

$$\frac{125 \times}{100} = \text{A}$$

**NAME PLATE DETAILS:**

**Primary**      **Secondary**

Rated Voltage :  
 Rated Current :  
 Rated Power :

Tabular Column





**Model Calculation:**


Output Power =  $W_2 \times$  Multiplication factor

Input Power =  $W_1 \times$  Multiplication factor

Output Power

$$\text{Efficiency } \eta = \frac{\text{input power}}{\text{output power}} \times 100 \text{ in } \%$$

$$\text{Regulation } \%R = \frac{V - V_L}{V} \times 100 \text{ in } \%$$

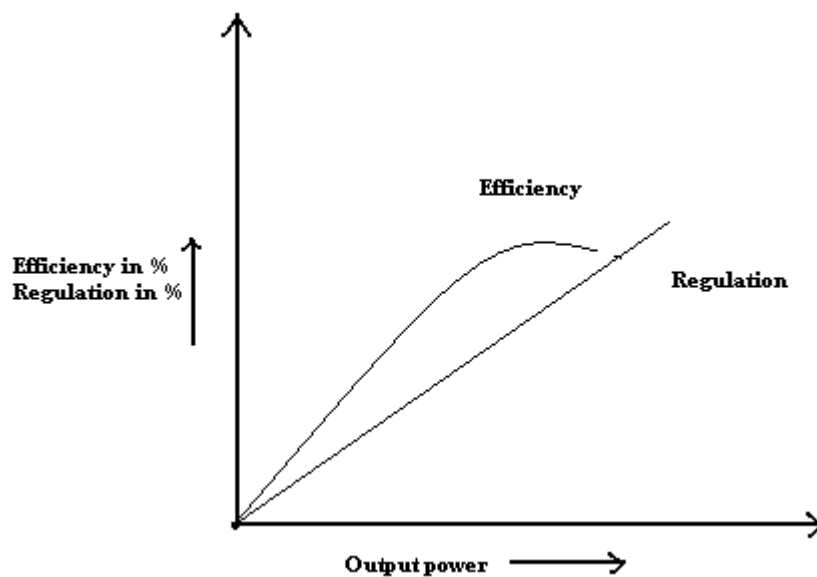**Model Graph:****Result:**

Thus the load characteristics of single Phase transformer was determined.

Ex. No: 9

Date:

### **Open circuit and short circuit tests on single phase transformer**

#### **AIM:**

To predetermine the efficiency and regulation of a transformer by conducting open circuit test and short circuit test and to draw equivalent circuit.

#### **APPARATUS REQUIRED:**

<b>Sno</b>	<b>Apparatus</b>	<b>Range</b>	<b>Type</b>	<b>Quantity</b>
1.	Voltmeter	(0-150)V	MI	1
2.	Ammeter	(0-2)A	MI	1
		(0-5)A		1
3.	Wattmeter	150 V, 5 A	UPF	1
		150 V, 5 A	LPF	
6.	Connecting wires	-	-	Required

#### **PRECAUTIONS:**

Auto Transformer should be in minimum voltage position at the time of

closing & opening DPST Switch.

## **PROCEDURE:**

### **OPEN CIRCUIT TEST:**


1. Connections are made as per the circuit diagram.
2. After checking the minimum position of Autotransformer, DPST switch is closed.
3. Auto transformer variac is adjusted get the rated primary voltage.
4. Voltmeter, Ammeter and Wattmeter readings on primary side are noted.
5. Auto transformer is again brought to minimum position and DPST switch is opened.

### **SHORT CIRCUIT TEST:**

1. Connections are made as per the circuit diagram.
2. After checking the minimum position of Autotransformer, DPST switch is closed.
3. Auto transformer variac is adjusted get the rated primary current.
4. Voltmeter, Ammeter and Wattmeter readings on primary side are noted.
5. Auto transformer is again brought to minimum position and DPST switch is opened.

## **CIRCUIT DIAGRAM**

### **Open circuit Test:**

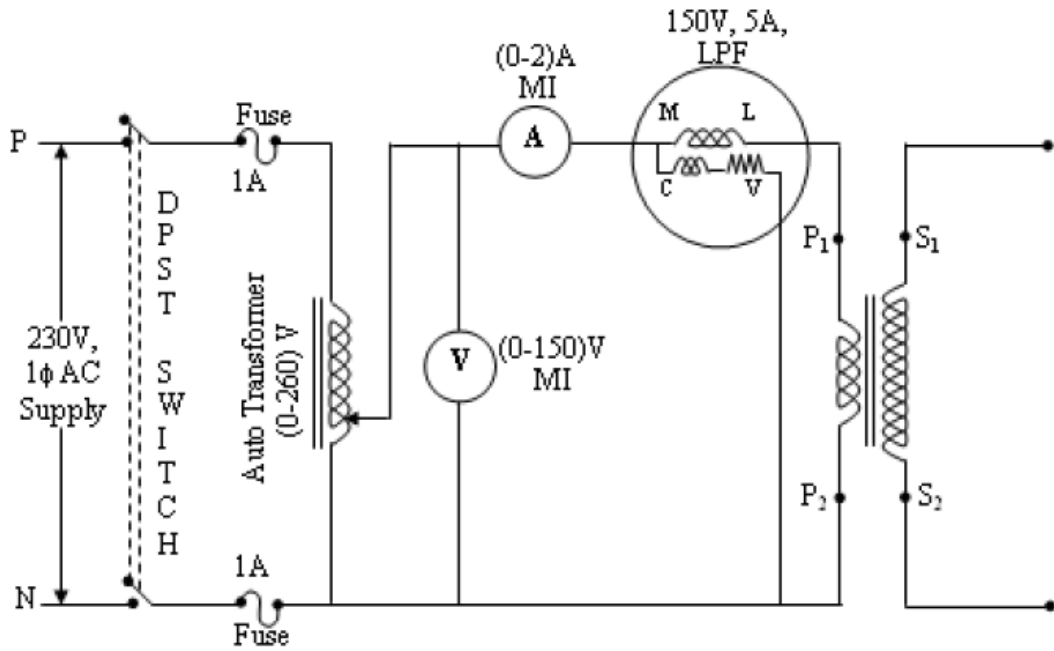

**FUSE RATING:**

10% of rated current

$$\frac{10 \times}{100} = \text{A}$$

**NAME PLATE DETAILS:**

Primary


Secondary

Rated Voltage :

Rated Current :

Rated Power :

**Short circuit Test:**

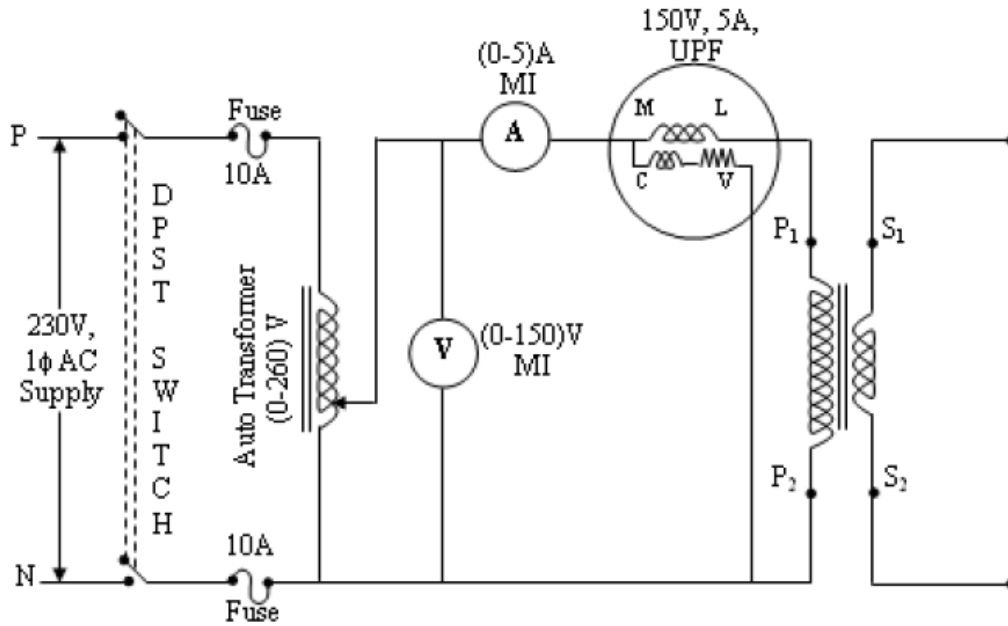

**FUSE RATING:**

125% of rated current

$$\frac{125 \times}{100} = \text{A}$$

**NAME PLATE DETAILS:**

Primary      Secondary

Rated Voltage :

Rated Current :

Rated Power :

**Tabular Column:**

**Open circuit test:**

Sno	Voltage $V_o$ in volts	Current $I_o$ in amps	$W_o$ in watts

**Short circuit test:**

Sno	Voltage $V_{sc}$ in volts	Current $I_{sc}$ in amps	$W_{sc}$ in watts

**Model calculation:**

Core loss:  $W_o = V_o I_o \cos \phi_o$

$$\cos \phi_o = \frac{W_o}{V_o I_o} \quad \phi_o = \cos^{-1} \frac{W_o}{V_o I_o}$$

$$I_w = I_o \cos \phi_o \text{ (Amps)} \quad I_\mu = I_o \sin \phi_o \text{ (Amps)}$$

$$R_o = \frac{V_o}{I_w} \Omega \quad X_o = \frac{V_o}{I_\mu} \Omega \quad R_{o2} = \frac{W_{sc}}{I_{sc}^2} \Omega$$

$$Z_{o2} = \frac{V_{sc}}{I_{sc}} \Omega \quad X_{o2} = (Z_o^2 - R_{o2}^2)^{1/2}$$

$$R_{o1} = \frac{R_{o2}}{K^2} \Omega \quad X_{o1} = \frac{X_{o2}}{K^2} \Omega \quad K = \frac{V_2}{V_1} = 2$$

$$\text{Efficiency, } \eta = \frac{x \times \text{KVA rating} \times 1000 \times \cos\phi}{(x \times \text{KVA rating} \times 1000 \times \cos\phi) + W_0 + x^2 W_{sc}}$$



$$\% \text{ Regulation} = \frac{x \times (I_{sc} R_{02} \cos\phi \pm I_{sc} X_{02} \sin\phi)}{V_2} \times 100$$

(+lagging, -leading)


**Tabular Column:**

X % load	Efficiency		Regulation	
	0.8 lag	0.8 lead	0.8 lag	0.8 lead
0.25				
Half load- 0.5				
0.75				
full load – 1				

**Model Graph**

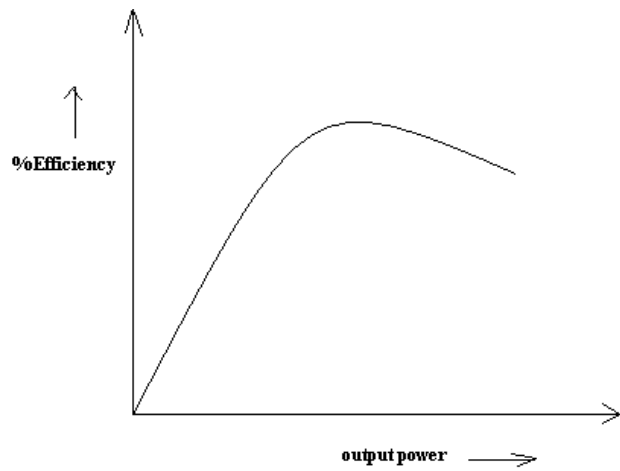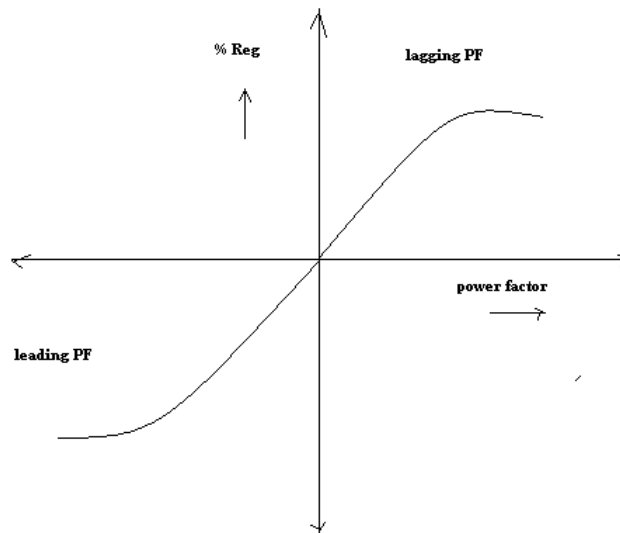

**Equivalent Circuit**

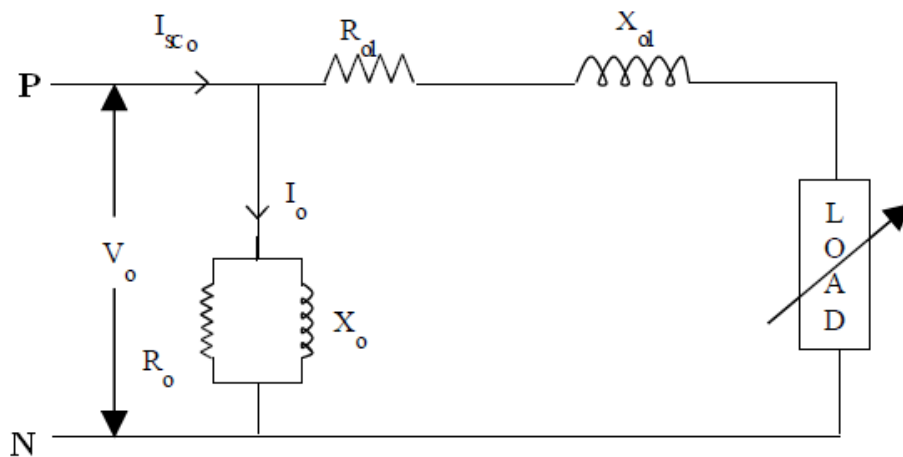



**RESULT:**

Thus the efficiency and regulation of a transformer is predetermined by conducting open circuit test and short circuit test and the equivalent circuit is drawn

Ex. No: 10

Date:

**SEPARATION OF NO-LOAD LOSSES IN SINGLE PHASE  
TRANSFORMER**

**AIM:**

To separate the eddy current loss and hysteresis loss from the iron loss of single phase transformer.

**TABULAR COLUMN:**

Sno	Apparatus	Range	Type	Quantity
1.	Voltmeter	(0-300)V	MI	1
2.	Ammeter	(0-2)A	MC	1

				1
3.	Wattmeter	300 V, 5 A	LPF	1
4.	Rheostat	700 $\Omega$ /1.5 A	Wire wound	1
4.	Connecting wires	-	-	Required

**PRECAUTIONS:**

1. The motor field rheostat should be kept at minimum resistance Position.
2. The alternator field rheostat should be kept at maximum resistance Position.

**PROCEDURE:**

1. Connections are given as per the circuit diagram.
2. Supply is given by closing the DPST switch.
3. The DC motor is started by using the 3 point starter and brought to rated speed by adjusting its field rheostat.
4. By varying the alternator filed rheostat gradually the rated primary voltage is applied to the transformer.
5. The frequency is varied by varying the motor field rheostat and the readings of frequency are noted and the speed is also measured by using the tachometer.
6. The above procedure is repeated for different frequencies and the readings are tabulated.

7. The motor is switched off by opening the DPST switch after bringing all the rheostats to the initial position.

**TABULAR COLUMN:**

SN O	Speed in rpm	Frequency F in Hz	Voltage V (Volts)	Wattmeter reading Watts	Iron loss Wi (Watts)	Wi / f Joules

**FORMULAE USED:**

Frequency,  $f = (P \cdot N_s) / 120$  in Hz

$P =$  No. of Poles,  $N_s =$  Synchronous speed in rpm.

Hysteresis Loss  $W_h = A \cdot f$  in Watts,  $A =$  Constant (obtained from graph)

Eddy Current Loss  $W_e = B \cdot f^2$  in Watts  $B =$  Constant (slope of the tangent drawn to the curve)


Iron Loss  $W_i = W_h + W_e$  in Watts

$W_i / f = A + (B \cdot f)$


Here the Constant A is distance from the origin to the point where the line cuts the Y- axis in the graph between  $W_i / f$  and frequency f.

The Constant B is  $\Delta (W_i / f) / \Delta f$

**Model Graph:**

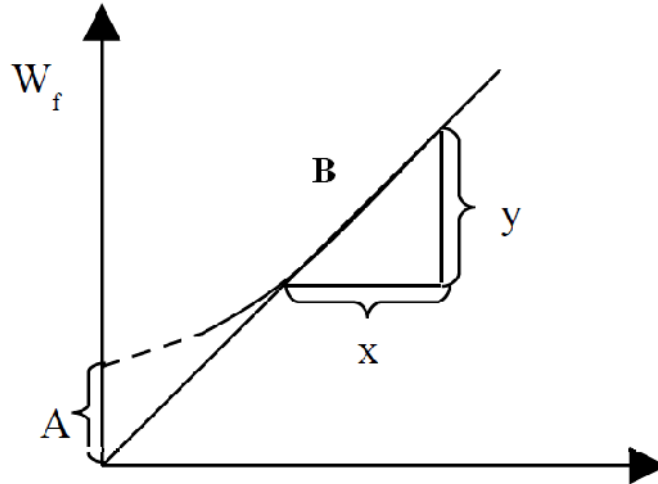

**CIRCUIT DIAGRAM:**

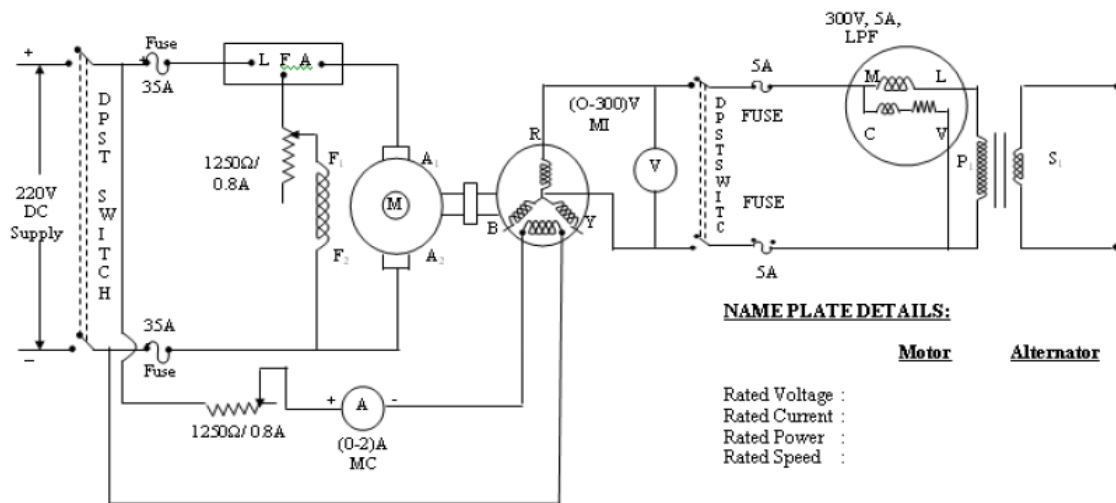

**NAME PLATE DETAILS:**

**Motor**      **Alternator**

Rated Voltage :  
 Rated Current :  
 Rated Power :  
 Rated Speed :

**FUSE RATING:**

125% of rated current

$$\frac{125 \times}{100} = \text{A}$$

**NAME PLATE DETAILS:**

**Primary**      **Secondary**

Rated Voltage :  
 Rated Current :  
 Rated Power :

**RESULT:**

Thus separation of eddy current and hysteresis loss from the iron loss on a single-phase transformer is conducted.

