

**KCT COLLEGE OF
ENGG AND
TECHNOLOGY**

DEPTT. OF ELECTRICAL ENGG.

LAB MANUAL

SUBJECT: SYNCHRONOUS MACHINES

INDEX

Exp No. 1 LOAD TESTS ON SQUIRELL CAGE INDUCTION MOTOR.

Exp. No.2 NO-LOAD AND BLOCKED ROTOR TEST ON SLIP RING INDUCTION NOTOR.

Exp No.3 LOAD TEST ON SINGLE PHASE INDUCTION MOTOR.

Exp. No.4 DETERMINE THE REGULATION OF THREE ALTERNATOR BY ZPF AND ASA METHODS.

Exp No.5 STUDY SYNCHRONIZING OF AN ALTERNATOR WITH BUS BARS

Exp No.6 TO DRAW V AND INVERTED V CURVES OF THREE PHASE SYNCHRONOUS MOTOR.

Exp. No.7 REGULATION OF THREE PHASE SALIENT POLE ALTERNATORBY CONDUCTING THE SLIP TEST.


Experiment No.: 1

LOAD TEST ON SQUIRREL CAGE INDUCTION MOTOR

Aim:

To study the performance of the machine when loaded and to plot the following characteristics of a squirrel cage induction motor.

Circuit Diagram:

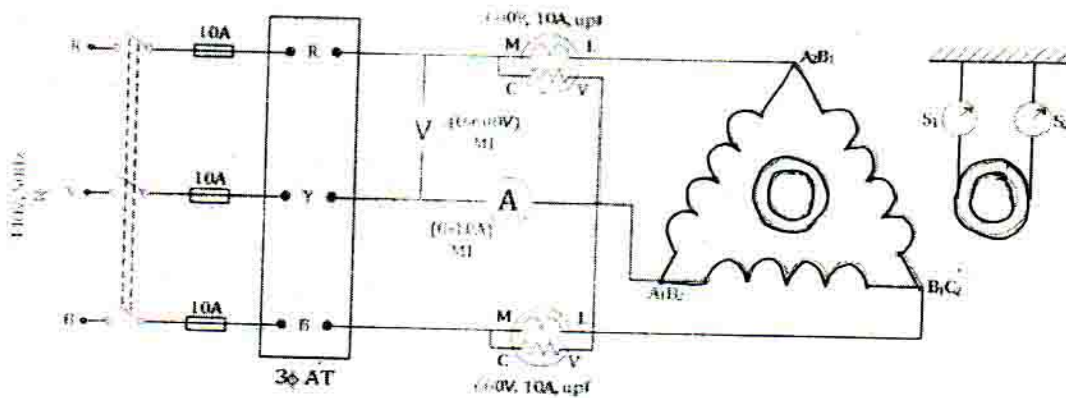

Precautions:

1. All the connections should be tight.
2. The autotransformer should be in minimum position initially.
3. The motor should be on no load at the time of starting.

Procedure:

1. Make the connections as shown in the circuit diagram.
2. After taking care of the precautions, switch on the supply.
3. Adjust the autotransformer till rated voltage is applied across the motor terminals.
4. Note down all the meter readings in no-load condition.
5. Increase the load in steps until the ammeter reads the rated current and note down all the meter reading for each applied load.
6. Reduce the load to zero, bring the autotransformer to the minimum position and switch off the supply.

Equations and Calculations:

Voltage $V = \dots\dots V$

Current $I = \dots\dots A$

$W_1 = \dots\dots W$

$W_2 = \dots\dots W$

I/P power = $W_1 - W_2 = \dots\dots W$

Speed $N = \dots\dots \text{rpm}$

$S_1 = \dots\dots \text{kg}$

$S_2 = \dots\dots \text{kg}$

• Torque $T = (S_1 - S_2)rg = \dots\dots \text{Nm}$

O/P power = $\frac{2\pi NT}{60} = \dots\dots W$

Power Factor $\cos\phi = \dots\dots$

Slip $s = \frac{N_s - N}{N_s} \times 100 = \dots\dots \%$

Efficiency $\eta = \frac{\text{O/P}}{\text{I/P}} \times 100 = \dots\dots \%$

Here r is the radius of the break drum and g is the acceleration due to gravity.

Result:

Observation Table:

Sl. No.	V_1 (V)	A_1 (A)	W_1 (W)	W_2 (W)	N (rpm)	S_1 (kg)	S_2 (kg)	I/P (W)	T (Nm)	o/p (W)	$\cos\phi$	%s	η
1	2	3	4	5	6	7	8	9	10	11	12	13	14

Experiment No.: 2

NO LOAD AND BLOCKED ROTOR TEST ON SLIP-RING INDUCTION MOTOR

Aim:

To conduct no load and blocked rotor test on slip-ring induction motor and to draw its equivalent circuit and circle diagram.

Machine Details:

Refer name plate of the machine.

Precautions:

1. The autotransformer should be in minimum position while switching on the supply.
2. The motor should not be on load while starting.

Procedure:

No-load test

1. After taking care of the precautions, switch on the supply.
2. Adjust the autotransformer gradually such that the rated voltage is applied to the stator.
3. Note down all the meter readings under no-load condition.
4. Reduce the autotransformer to minimum position.
5. Switch off the supply.

Blocked rotor test

1. After taking care of the precautions, switch on the supply.
2. Adjust the autotransformer till the rated current flows through the stator.
3. Take all the meter readings.
4. Reduce the autotransformer to minimum position.
5. Switch off the supply.

Equations and Calculations:

$$\text{Voltage } V = \dots \text{ V}$$

$$\text{Current } I = \dots \text{ A}$$

$$W_1 = \dots \text{ W}$$

$$W_2 = \dots \text{ W}$$

$$\text{I/P power} = W_1 + W_2 = \dots \text{ W}$$

$$\text{Speed } N = \dots \text{ rpm}$$

$$S_1 = \dots \text{ kg}$$

$$S_2 = \dots \text{ kg}$$

$$\text{Torque } T = (S_1 - S_2)rg = \dots \text{ Nm}$$

$$\text{O/P power} = \frac{2\pi NT}{60} = \dots \text{ W}$$

$$\text{Power Factor } \cos\phi = \dots$$

$$\text{Slip } s = \frac{N_s - N}{N_s} \times 100 = \dots \%$$

$$\text{Efficiency } \eta = \frac{\text{O/P}}{\text{I/P}} \times 100 = \dots \%$$

Here r is the radius of the break drum and g is the acceleration due to gravity.

Circuit Diagram:

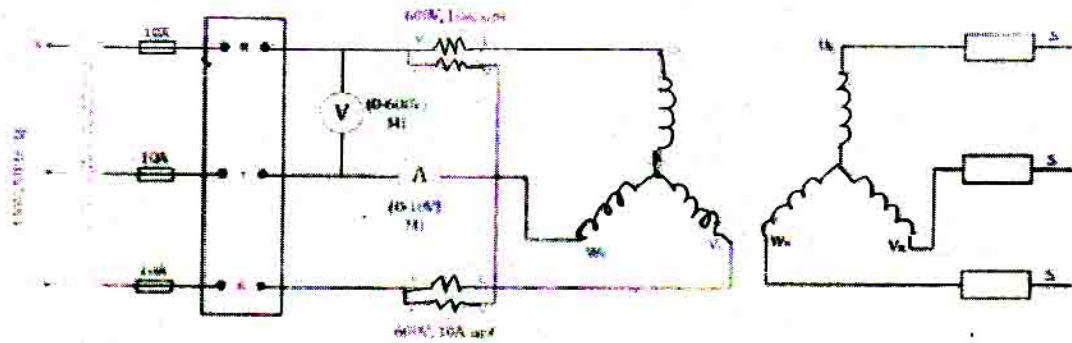


Figure 1: Circuit diagram for no-load test.

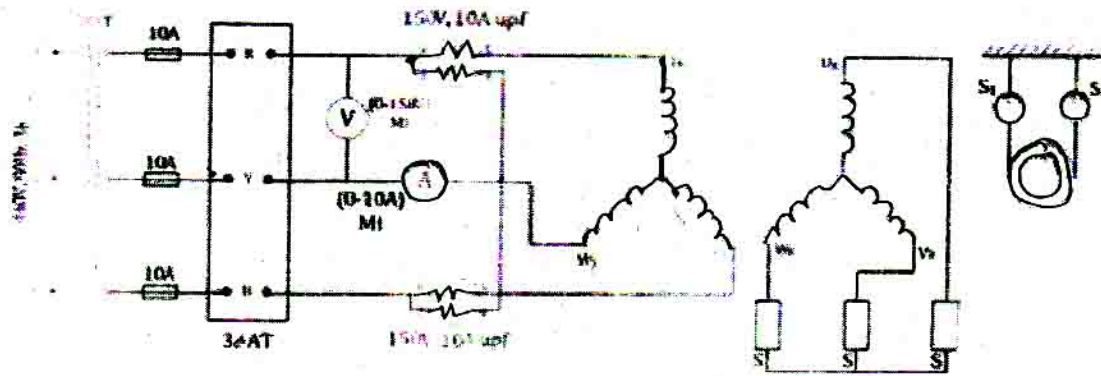


Figure 2: Circuit diagram for blocked rotor test.

Observation Table:

No-load test

Sl. No.	V_0 (V)	I_0 (A)	W_1 (W)	W_2 (W)	W_0 (W)
1					
2					
3					
4					
5					
6					

Blocked rotor test

Sl. No.	V_{sc} (V)	I_{sc} (A)	W_1 (W)	W_2 (W)	W_{sc} (W)
1					
2					
3					
4					
5					
6					

Equations and Calculations:

From no-load test

Supply voltage $V_0 = \dots\dots\dots$ V
 Circuit current $I_0 = \dots\dots\dots$ A
 No-load power $W_0 = W_1 + W_2 = \dots\dots\dots$ W

$$\cos \phi_0 = \frac{W_0}{\sqrt{3}V_0 I_0} = \dots\dots\dots$$

 Magnetising current $I_w = I_0 \sin \phi_0 = \dots\dots\dots$ A
 Working current $I_w = I_0 \cos \phi_0 = \dots\dots\dots$ A

$$R_0 = \frac{V_0}{I_w} = \dots\dots\dots \Omega$$

$$X_0 = \frac{V_0}{I_w} = \dots\dots\dots \Omega$$

From blocked rotor test

Supply Voltage $V_{sc} = \dots\dots\dots$ V
 Circuit current $I_{sc} = \dots\dots\dots$ A
 Power consumed $W_{sc} = W_1 + W_2 = \dots\dots\dots$ W

$$Z_{01} = \frac{V_{sc}}{I_{sc}} = \dots\dots\dots \Omega$$

$$R_{01} = \frac{W_{sc}}{3I_{sc}^2} = \dots\dots\dots \Omega$$

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \dots\dots\dots \Omega$$

Experiment No.: 3

LOAD TEST ON SINGLE PHASE INDUCTION MOTOR

Aim:

To conduct load test on a single phase induction motor and to plot the following characteristics.

Precautions:


1. All the connections should be tight.
2. The motor should not be on load while starting.

Procedure:

1. Close DPST and start the motor on no load at rated voltage
2. Note down all the meter readings at no load.
3. Gradually apply the load in steps till the ammeter reads rated current. Note down all the meter readings for each load.
4. Gradually decrease the load to zero and switch off the supply.

Circuit Diagram:

Circuit Diagram:

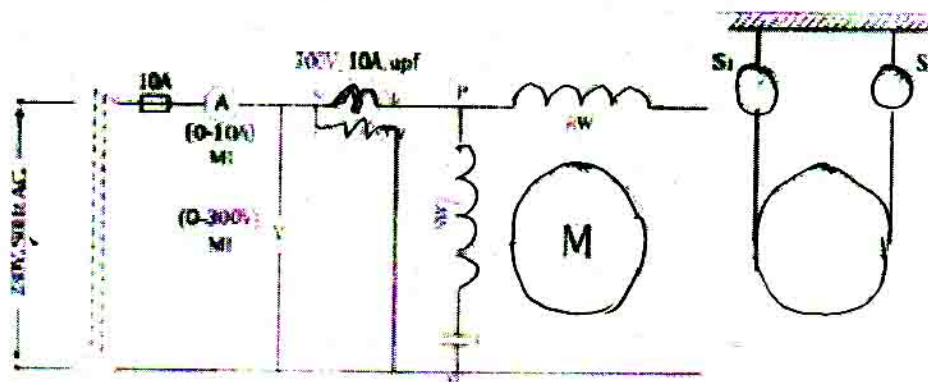

Observation Table:

Sl. No.	V ₁ (V)	A ₁ (A)	W ₁ (W)	N (rpm)	S ₁ (kg)	S ₂ (kg)	T (Nm)	O/P (W)	cos φ	η
1										
2										
3										
4										
5										
6										

Equations and Calculations:

Voltage V = V

Current I = A

I/P power = W₁ = W

Speed N = rpm

S₁ = kg

S₂ = kg

Torque T = (S₁ - S₂)rg = Nm

O/P power = $\frac{2\pi NT}{60}$ = W

Power Factor cos φ =

Efficiency η = $\frac{O/P}{I/P} \times 100 = \dots\dots\%$

Here r is the radius of the break drum and g is the acceleration due to gravity.

Result:

Experiment No.: 4

AIM:

The aim of the experiment is to predetermine the regulation of three phase alternator by ZPF and ASA methods.

APPARATUS REQUIRED:

S.NO	NAME OF THE APPARATUS	RANGE	TYPE	QUANTITY
1.	Ammeter	(0-2)A	MC	1
2.	Ammeter	(0-10)A	MC	1
3.	Ammeter	(0-10)A	MC	1
4.	Ammeter	(0-10)A	MI	1
5.	Voltmeter	(0-600)V	MI	1
6.	Voltmeter	(0-75)V	MC	1
7.	Rheostat	370Ω,1.5A	Wire wound	1
8.	Rheostat	270Ω,1.5A	Wire wound	1
9.	Rheostat	1000Ω,1A	Wire wound	1
10.	Inductive load	3 phase	-	1
11.	Tachometer	-	Digital	1
12.	Connecting wires	-	-	As required

FORMULA USED:

$$1. \text{ Percentage regulation} = \frac{E_o - V_{rated}}{V_{rated}} * 100$$

(For both ZPF and ASA method)

THEORY:

ZERO POWER FACTOR METHOD:

ZPF method is based on the separation of armature leakage reactance and armature reaction effects. To determine armature leakage reactance and armature reaction mmf separately, two tests are performed on the alternator. The two tests are 1. Open circuit test 2. Short circuit test 3. Zero power factor tests

PROCEDURE TO DRAW THE POTIER TRIANGLE: (ZPF METHOD)

1. Draw the open circuit characteristics curve (Generated voltage per phase Vs field current)
2. Mark the point A at X axis, which is obtained from short circuit test with full load armature current.
3. From the ZPF test, mark the point B for the field current to the corresponding rated armature current and the rated voltage.

4. Draw the ZPF curve which is passing through the point A and B in such a way parallel to the open circuit characteristic curve.
5. Draw the tangent for the OCC from the origin (Air gap line).
6. Draw the line BC from B towards Y axis which is parallel and equal to OA.
7. Draw the parallel line for the tangent from c to the OCC curve.
8. Join the point B and D also draws a perpendicular line DE to BC. DE = Armature leakage reactance drop
BC = Armature reaction excitation

RESULT:

TABULAR COLUMN:

OPEN CIRCUIT TEST:

S.NO	Field Current (If) (amps)	Open Circuit Voltage (V_{OL}) (volts)	Open Circuit Phase Voltage (V_{oph}) (volts)

SHORT CIRCUIT TEST:

S.NO	Field Current (If) (amps)	Short Circuit Current (120 to 150% of rated current) (Isc) (amps)

ZERO POWER FACTOR TEST:

S.NO	Field current (If) (amps)	Rated armature current (Ia) (amps)	Rated armature Voltage (V) (volts)	W ₁ Obs Act (watts)	W ₂ Obs Act (watts)	Total power (W ₁ +W ₂) (watts)

ARMATURE RESISTANCE Ra:

S.NO	Armature Current (I) (amps)	Armature Voltage(V) (volts)	Armature Resistance Ra= V/I ohm

Experiment No.: 5

AIM:

To study the synchronizing of an alternator with bus bars.

APPARATUS:

- 1) Thyristor Rectifiers - 2
- 2) Voltmeters - 2 No
- 3) 3 lamp sets

MACHINE SPECIFICATION:

3.5 KVA, 415V, 4.2A, 1500R.P.M., 3- Φ alternator.

THEORY:

The operation of connecting alternator in loads with another alternator or with common bus bar is known as synchronizing. For proper synchronizing of alternator the following three conditions must be satisfied.

- 1) The terminal voltage of the incoming machine must be same as bus bar voltage.
- 2) The speed of the incoming machine must be same as its frequency must be same as bus bar frequency.
- 3) The phase of the alternator voltage must be identical with the phase of the bus bar voltage. It means that the switch must be closed at the instant the two voltages have common phase relationship. However, it is necessary, that the incoming alternator should have the same phase sequence. In this method, three lamps are used. The transposition of two lamps as suggested by Siemens helps us to ascertain whether the incoming machine is running too slow or too fast. If lamps are connected symmetrically then they would dark off and glow up simultaneously. Lamp L1 is connected between R & R', L2 is between Y & B' and L3 between Y' & B.


If incoming alternator is running faster than bus bar alternator then the voltage star R'Y'B' will appear to rotate anti-clockwise w.r.t. the bus bar star voltage RYB at speed corresponding to the difference of frequencies between machine frequency and the bus bar frequency as shown in figure. If the incoming machine is faster then voltage across L1 is RR' and is seen to be increasing while the voltage across Y1 B is seen to be increasing while the voltage across Y & B' decreases. Reverse thing happens if the incoming machine is slower. There are three methods of synchronizing the alternator.

1) Dark lamp method: Suppose m/c-2 is to be synchronized with the bus bars to which m/c is already connected. This is done with the help of two lamps L1 and L2 connected as shown in fig. It should be noted E1 and E2 are in phase relative the external ckt. and are in direct phase opposition in no-load ckt. If the frequency of the two alternators is different there will be a phase difference between voltages. This phase diff. continuously changes with the change in their frequency. Here in this method the lamps will glow and become dark time to time and the frequency of flicker will depend upon relative difference of frequency between the two. Darkness indicates two voltages are in exact phase-opposition. Synchronizing is done at the middle of the dark period.

2) One dark and two bright lamp method: In a three phase alternator it is necessary to synchronize only one phase two phase coil can be synchronized automatically earlier in the order 3,2,1, etc. which is just after the another reverse. At the first synchronizing, is done at the moment the unglowed lamp L1 is in the middle of the dark period. It will be noticed

that when the uncrossed lamp L1 is dark the other two voltage lamps L2 & L3 are equally bright. Hence, this method also known as-two bright and one dark lamp method.

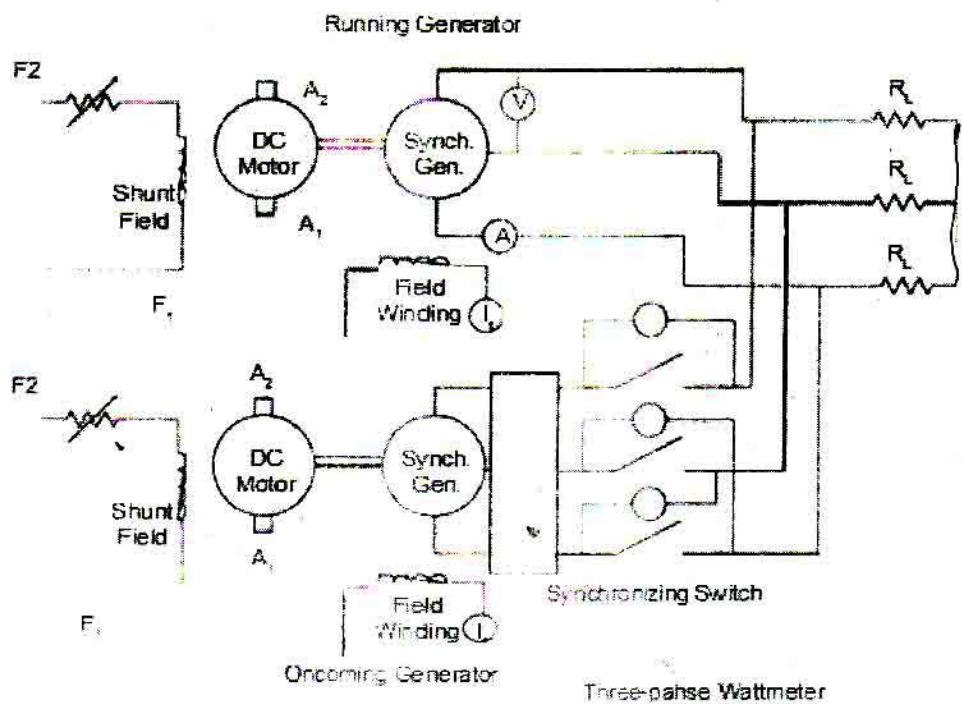3) Synchroscope method : To eliminate the scheme of (parallel) personal judgment in routine operation of alternators, the machine are synchronized by synchroscope. It consists of three stationary coils and rotating iron valve which is attached to a pointer. Out of three coils a pair is connected to bus-bars and other to the corresponding m/c terminals. Potential transformer are generally used in case of high voltage machines. The pointer moves to one side or the other depending on whether the incoming machine is faster or slower. For correct speed the pointer points vertically up



PROCEDURE:

- 1] Connect the ckt. as shown in ckt. diagram. Connect respective phase in sequential order.
- 2] Give excitation to the alternator and adjust the value to be of bus bar voltage
- 3] Adjust the speed of the alternator such that frequency is 50 Hz.

Adjust the speed of the alternator such that the lamp L1 is dark while the other two lamps L2 and L3 are equally bright.

Close the switch 's' and synchronize the m/c without jerk.

CONCLUSION:

We can conclude that by using three methods mentioned above we can synchronize an incoming alternator to the bus-bars keeping in mind the necessary precautions.

Experiment No.: 6

AIM:

The aim of the experiment is to draw the V and inverted V curves of three phasesynchronous motor.

APPARATUS REQUIRED:

S.NO	NAME OF THE	RANGE	TYPE	QUANTITY
	APPARATUS			
1.	Ammeter	(0-10) A	MI	1
2.	Ammeter	(0-2) A	MC	1
3.	Voltmeter	(0-600) V	MI	1
4.	Wattmeter	500V, 10 A	Double element	1
5.	Rheostat	500 Ω , 1.2 A	Wire wound	2
6.	Tachometer		Digital	1
7.	3 Φ Auto transformer	415/(0-470)V		1
8.	Connecting wires			As required

THEORY:

Synchronous motor is constant speed motor which are not self starting in nature, sothat we have to start this motor by any one of the following starting methods

1. Pony motor method starting

2. Auto induction starting

3. DC exciter starting

4. Damper winding method of starting By construction there is no difference between a synchronous generator and synchronous motor. It is capable of being operated under wide range of power factor, hence it can be used for power factor correction. The value of excitation for which back emf is equal to applied voltage is known as 100% excitation. The other two possible excitations are over excitations and under excitation if the back emf is more or less to the applied voltage respectively. The variations of armature current with field current are in the form of V curves and the variation of power factor with field current are in the form of Inverted V curves.

PRECAUTIONS:

1. The potential divider should be in the maximum position

2. The motor should be started without any load.

3. Initially TPST switch is in open position.

PROCEDURE:

1. Note down the name plate details of motor

2. Connections are given as per the circuit diagram.

3. Close the TPST switch.

4. By adjusting the auto transformer from minimum position to maximum position the rated supply is given to the motor. The motor starts as an induction motor.

5. In order to give the excitation to the field for making it to run as the synchronous motor close the DPST switch

6. By varying the field rheostat note down the excitation current, armature current and the power factor for various values of excitation.

7. The same procedure has to be repeated for loaded condition. 8. Later the motor is switched off and the graph is drawn

GRAPH:

The graph is drawn for 1. Armature current Vs Excitation current
2. Power Factor Vs Excitation current

TABULAR COLUMN:

Armature voltage:

Without load:

S.no	Excitation current (If) (Amps)	Armature current (Ia) (Amps)	Power factor (CosΦ)

Experiment No.: 7

AIM

The aim of the experiment is to predetermine the regulation of three phase salient pole alternator by conducting the slip test

APPARATUS REQUIRED:

S.NO	NAME OF THE APPARATUS	RANGE	TYPE	QUANTITY
1.	Ammeter	(0-5) A	MI	1
2.	Ammeter	(0-5) A	MC	1
3.	Voltmeter	(0-150) V	MI	1
4.	Voltmeter	(0-150)V	MC	1
5.	Rheostat	300Ω, 1.5A	Wire wound	1
6.	3 Φ Auto transformer			1
7.	Tachometer			1
8.	Connecting wires			As required

FORMULA USED:

1. Armature Resistance $R_a = 1.6 * R_{dc}$
2. Direct impedance per phase (Z_d) = V_{min} / I_{max} in Ω
3. Quadrature axis impedance per phase (Z_q) = V_{max} / I_{min} in Ω
4. Direct axis reactance per phase (X_d) = $\sqrt{Z_d^2 - R_a^2}$ in Ω
5. Quadrature axis reactance per phase (X_q) = $\sqrt{Z_q^2 - R_a^2}$ in Ω
6. Percentage Regulation = $(E_o - V_{rated} / V_{rated} * 100$
7. $E_o = V_t \cos \delta - I_q R_a - I_d X_d$ (Motoring)
8. $E_o = V_t \cos \delta + I_q R_a + I_d X_d$ (Generating)
9. $\delta = \Psi - \Phi$ (Generator)
10. $\delta = \Phi - \Psi$ (Motor)
11. $\Psi = (\tan^{-1} (V_t \sin \Phi + I_a X_q / V_t \cos \Phi + I_a R_a))$ For generating mode
For Motoring mode

THEORY:

In non salient pole alternators air gap length is constant and reactance is also constant. Due to this the mmfs of armature and field act upon the same magnetic circuit all the time hence can be added vector ally. But in salient pole alternators the length of the air gap varies and reluctance also varies. Hence the armature flux and field flux cannot vary sinusoid ally in the air gap. So the reluctance of the magnetic circuit on which mmf act is different in case of salient pole alternators. This can be explained by two reaction theory

PRECAUTIONS:

1. The motor field rheostat should be kept in minimum resistance position
2. The alternator field should be kept open throughout the experiment.
3. The direction of rotation due to prime mover and due to the alternator run as a motor should be same.

4. Initially all the switches are kept open.

PROCEDURE:

1. Note down the name plate details of motor and alternator
2. Connections are given as per the circuit diagram
3. Give the supply by closing the DPST switch
4. Using the three point starter start the motor to run at the synchronous speed by varying the motor field rheostat at the same time check whether the alternator field has opened or not
5. Apply 20% to 30% of the rated voltage to the armature of the alternator by adjusting the autotransformer
6. To obtain the slip and maximum oscillations of pointers, the speed is reduced slightly lesser than the synchronous speed
7. Maximum current, minimum current, maximum voltage and Minimum voltage are noted.
8. Find out the direct and quadrature axis impedance (Z_d, Z_q).

RESULT:

**TABULAR COLUMN: TO FIND OUT THE DIRECT AXIS IMPEDANCE (Z_d) : Speed of the alternator:
Minimum Voltage applied to the stator: (Nearly 20% to 30% of rated voltage)**

S.NO	Minimum current per phase (I_{min}) (amps)	Maximum Voltage per phase (V_{max}) (volts)	Direct axis impedance per phase (Z_d) (Ohms)	Direct axis Reactance per phase (X_d) (Ohms)

TO FIND OUT THE QUADRATURE AXIS IMPEDANCE (Z_q):

S.NO	Maximum current per phase (I_{max}) (amps)	Minimum Voltage per phase (V_{min}) (volts)	Quadrature axis impedance per phase (Z_d)	Quadrature axis Reactance per phase (X_d)
------	--	---	---	---

			(Ohms)	(Ohms)

Experiment No.: 8

AIM:

The aim of the experiment is to conduct the no load and blocked rotor test on single phase induction motor and to draw the equivalent circuit

APPARATUS REQUIRED:

S.NO	NAME OF THE APPARATUS	RANGE	TYPE	QUANTITY
1.	Ammeter	(0-10) A	MI	1

2.	Ammeter	(0-10) A	MC	1
3.	Ammeter	(0-10) A	MI	1
4.	Voltmeter	(0-300) V	MI	1
5.	Voltmeter	(0-150) V	MI	1
6.	Voltmeter	(0-75) V	MC	1
7.	Wattmeter	300V, 10 A	LPF	1
8.	Wattmeter	150V, 10 A	UPF	1
9.	Tachometer	-	Digital	1
10.	1 Φ Auto transformer Connecting wires	230/(0-270) V		1 As required

FORMULA USED:**NO LOAD TEST:**

$$1. \text{No load power factor } (\cos\phi_0) = W_0 / V_0 I_0$$

Where W_0 = No load power in watts V_0

V_0 - No load voltage in volts. I_0 - No load current in amps.

$$2. \text{Working component current } (I_w) = I_0 \cos\phi_0 \text{ amps}$$

$$3. \text{Magnetizing component current } (I_m) = I_0 \sin\phi_0 \text{ amps}$$

$$4. \text{No load resistance } R_0 = V_0 / I_w \text{ ohm}$$

$$5. \text{No load reactance } X_0 = V_0 / I_m \text{ ohm}$$

BLOCKED ROTOR TEST:

$$6. \text{Motor equivalent impedance referred to stator } Z_{sc} = (V_{sc} / I_{sc}) \text{ ohm}$$

$$7. \text{Motor equivalent resistance referred to stator } R_{sc} = Z_{sc} \cos\phi_{sc} \text{ ohm} = W_{sc} / I_{sc}^2 \text{ ohm}$$

$$8. \text{Power factor } \cos\phi_{sc} = W_{sc} / V_{sc} I_{sc}$$

$$9. \text{Motor equivalent reactance referred to stator } X_{sc} = \sqrt{Z_{sc}^2 - R_{sc}^2} \text{ ohm}$$

$$10. \text{Rotor resistance referred to stator } R_2' = R_{sc} - R_1 \text{ ohm}$$

$$11. \text{Rotor reactance referred to stator } X_2' = X_{sc} / 2 = X_1 \text{ ohm} \quad \text{where } R_1 = R_{ac} = 1.6 * R_{dc} \quad R_1 = \text{stator resistance} \quad X_1 = \text{stator reactance}$$

$$12. \text{Magnetizing reactance } X_m = 2(X_0 - X_1 - X_2' / 2)$$

$$13. \text{Slip } s = (N_s - N) / N_s \quad N_s = \text{synchronous speed in rpm} \quad N = \text{speed of the motor in rpm}$$

THEORY:

27

The equivalent circuit of a single phase induction motor can be developed by using double field revolving theory. By using the equivalent circuit the performance of the single phase induction motor can be obtained. The single phase induction motor can be visualized to be made of single stator winding and two imaginary rotors. The developing torques of the induction motor is forward torque and backward torque. When the single phase induction motor is running in the direction of forward revolving field at a slip S , then the rotor currents induced by the forward field has frequency $s f$. The rotor mmf rotates at slip speed with respect to the rotor but at synchronous speed with respect to the stator. The resultant forward stator flux and the rotor flux produce a forward air gap flux. This flux induces the voltage in rotor. Thus due to the forward flux, the rotor circuit referred to stator has an impedance of $R_2' / 2s + jX_2' / 2$. The backward flux induces a current in the rotor at a frequency $(2-s)f$. The corresponding rotor mmf rotates in the air gap at synchronous speed in the backward direction. The resultant backward stator flux and the rotor flux produce a backward air gap flux. This flux induces the voltage in rotor. Thus due to backward flux the rotor circuit referred to stator has an impedance of $R_2' / 2(2-s) + jX_2' / 2$

NO LOAD TEST OR OPEN CIRCUIT TEST:

No load test is performed to determine the no load current, no load power factor, windage and friction losses, no load input and no load resistance and reactance. Since there is no power output on no load, the power supplied to the stator furnishes its core loss and the friction and windage losses in the rotor.

BLOCKED ROTOR TEST OR SHORT CIRCUIT TEST:

It is also known as locked rotor or short circuit test. This test is used to find the short circuit current with normal voltage applied to stator, power factor on short circuit, total leakage reactance and resistance of the motor as referred to stator and full load copper loss.

PRECAUTIONS:

1. The auto transformer should be kept at minimum voltage position.

PROCEDURE:

1. Connections are made as per the circuit diagram.
2. For no load test by adjusting autotransformer apply rated voltage and note down the ammeter, voltmeter and wattmeter readings. In this test the rotor is free to rotate
3. For blocked rotor test by adjusting autotransformer apply rated current and note down the ammeter, voltmeter and wattmeter readings. In this test the rotor is blocked.
4. After that make the connections to measure the stator resistance as per the circuit diagram
5. By adding the load through the loading rheostat note down the ammeter, voltmeter readings for various values of load.

RESULT:

47.7

TABULAR COLUMN:

NO LOAD TEST:

Speed of the induction motor:

Multiplication Factor:

S.no	No load current (I_o)	No Load Voltage (V_o)	No load Power		Total No load Power
	(Amps)	(Volts)	W_1	W_2	W_1+W_2
	(Amps)	(Volts)	(Watts)		(Watts)

BLOCKED ROTOR TEST:

Speed of the induction motor:

Multiplication Factor:

S.no	Short circuit current (I_{sc})	Short circuit Voltage (V_{sc})	Short circuit Power		Total Power
	(Amps)	(Volts)	W_1	W_2	W_1+W_2
	(Amps)	(Volts)	(Watts)		(Watts)

ARMATURE RESISTANCE R_a :

S.NO	Armature Current (I) (amps)	Armature Voltage(V) (volts)	Armature Resistance $R_a = V/I$ ohm